



Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671


[1]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Analog Electronic Circuits

Prof. Mor M. Peretz

The Center for Power Electronics and Mixed-Signal IC
Department of Electrical and Computer Engineering
Ben-Gurion University of the Negev, *ISRAEL*

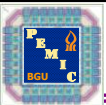Emails: morp@bgu.ac.ilWebsite: <http://www.ee.bgu.ac.il/~pemic>
<http://www.ee.bgu.ac.il/~analog>

Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[2]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Lesson #4 Outline

- Slew-rate (summary)
- Input Impedances
 - Differential
 - Common-Mode
- CMRR
- Effect of feedback on impedances
 - Blackman's theorem
 - Output
 - Current and voltage feedback
 - Input
 - Series and parallel summation
- Instrumentation amplifier
- Stability




Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[3]


THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Transient response Slew-Rate

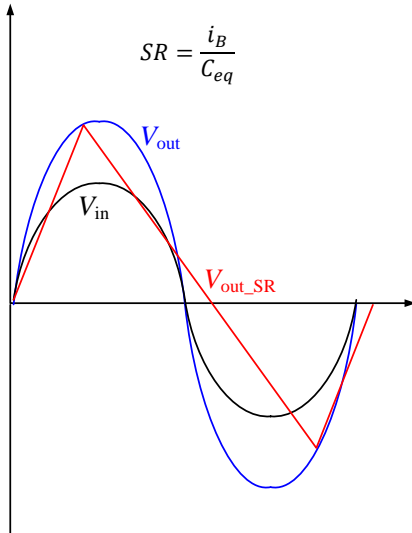

Sine wave
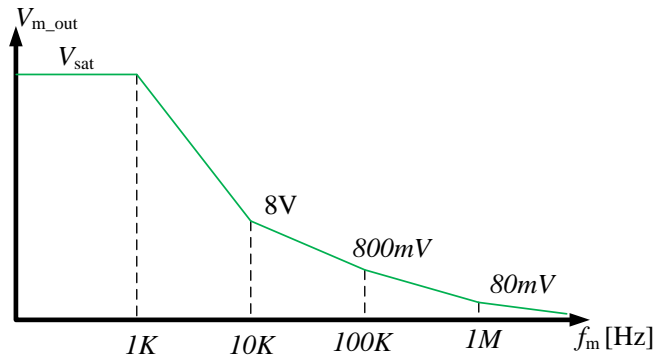
$$V_{m_out} = \min\left(\frac{SR}{2\pi f_m}, V_{sat}\right)$$





Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[4]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Input Impedances

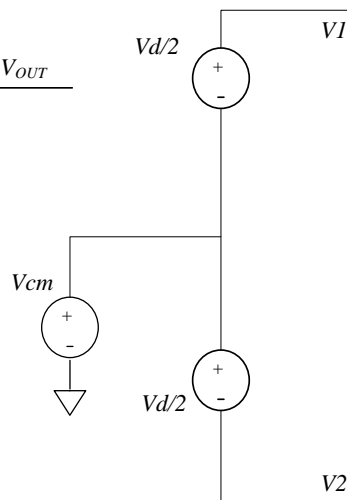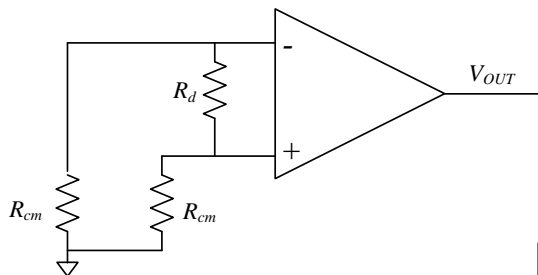

$$V_{cm} = \frac{V_1 + V_2}{2}$$

$$V_d = V_1 - V_2$$



Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671



[5]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Input Impedances Differential

$$h_{ie} = \frac{V_T}{I_e} (h_{fe} + 1)$$
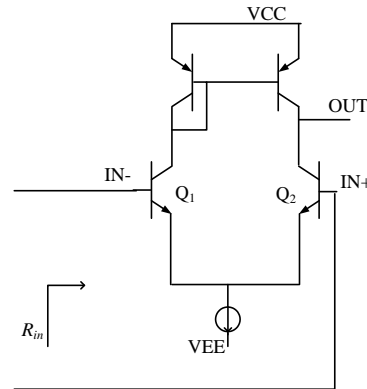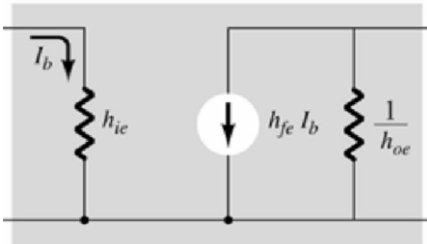
$$R_d = 2h_{ie} = 2 \frac{V_T}{I_e} (h_{fe} + 1)$$





Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[6]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Input Impedances Common-mode

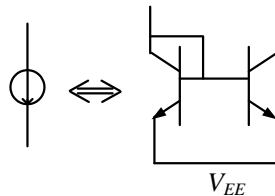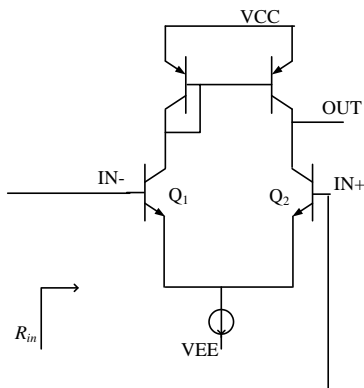

$$R_e = \frac{1}{h_{oe}}$$

$$R_{cm} = 2R_e (h_{fe} + 1)$$




Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[7]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Common-Mode Rejection Ratio (CMRR)

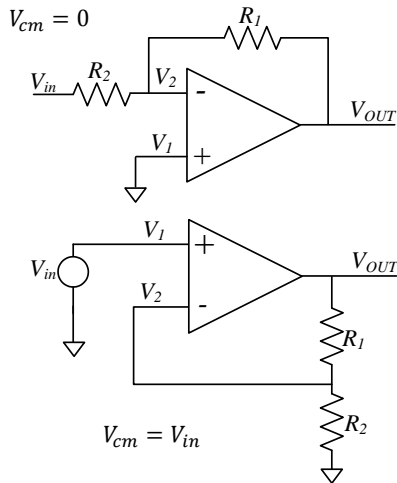

$$CMRR \equiv \frac{A_d}{A_{cm}} = \frac{A_d A_2 A_3}{A_{cm} A_2 A_3}$$

$$V_{cm} = \frac{V_1 + V_2}{2}$$

$$V_d = V_1 - V_2$$

$$V_{out,cm} = A_{cm} V_{cm} = A_{cm} \frac{V_1 + V_2}{2}$$




Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[8]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Common-Mode Rejection Ratio (CMRR)

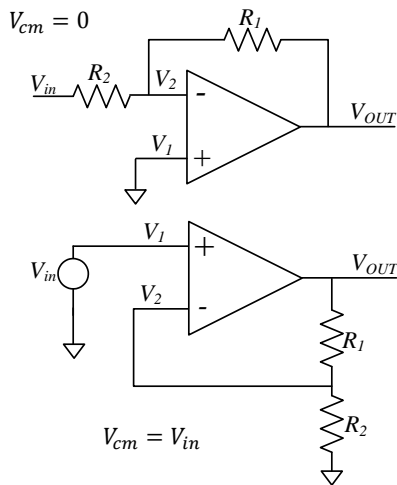

$$V_{out} = A_{cm} V_{cm} + A_d V_d$$

$$\frac{V_{out}}{A_d} = \frac{V_{cm}}{CMRR} + V_d \quad \text{Reflected to input (as done to ALL non-idealities)}$$



Prof. Mor M. Peretz


Analog Electronic Circuits 361-1-3671

[9]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY


Blackman's Theorem
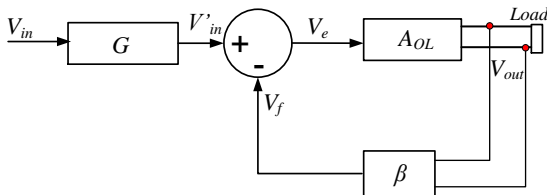
$$Z_F = Z_{NF} \frac{1 + \beta A_{SC}}{1 + \beta A_{OC}}$$



Voltage feedback

$$Z_F = \frac{Z_{NF}}{(1 + \beta A)}$$

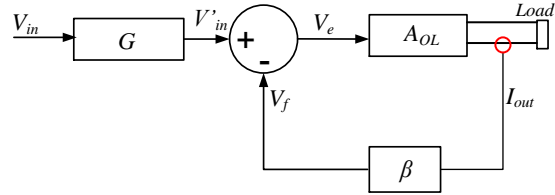

Current feedback

$$Z_F = Z_{NF} (1 + \beta A)$$



Prof. Mor M. Peretz


Analog Electronic Circuits 361-1-3671

[10]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY


Effect of feedback Output impedance

Voltage feedback

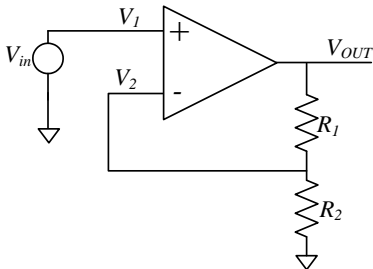

$$Z_{out_F} = R_0 \frac{1 + \beta A_{SC}}{1 + \beta A_{OC}}$$



Current feedback

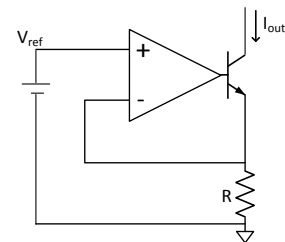

$$Z_{out_F} = R_0 \frac{1 + \beta A_{SC}}{1 + \beta A_{OC}}$$




Effect of feedback Example

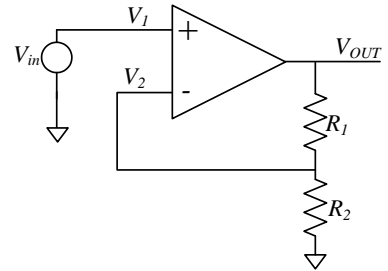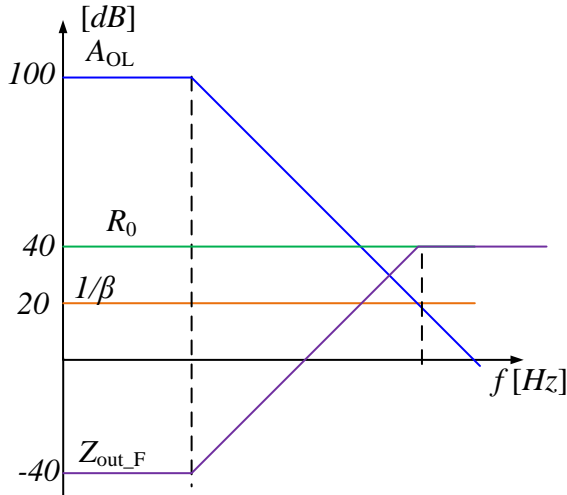




R1=10k
R2=1k
R0=100



Linear regulator Low-Drop Out (LDO)

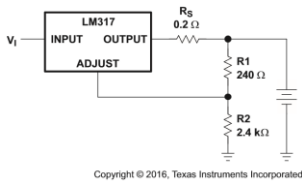


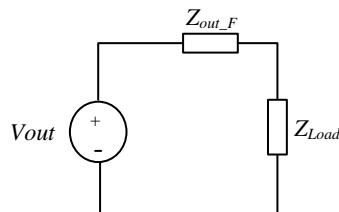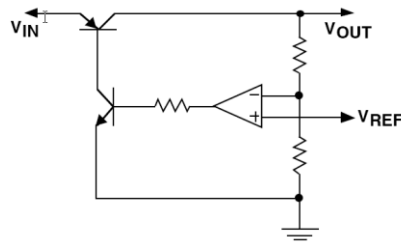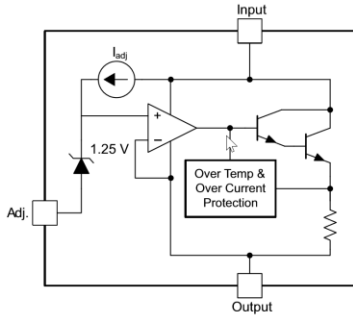Copyright © 2016, Texas Instruments Incorporated






Effect of feedback Input impedance

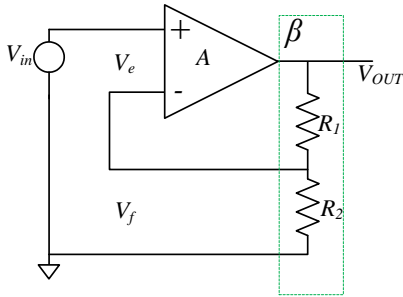

Series (voltage) summation

$$Z_{in_F} = Z_{NF}(1 + \beta A)$$

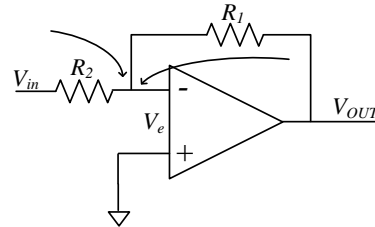


Parallel (current) summation


$$Z_{in_F} = \frac{Z_{NF}}{(1 + \beta A)}$$




Input Impedances

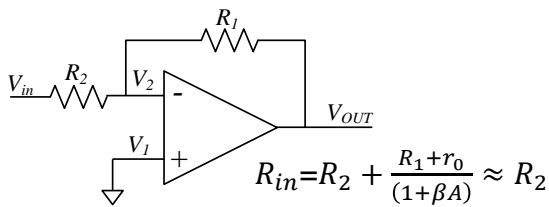
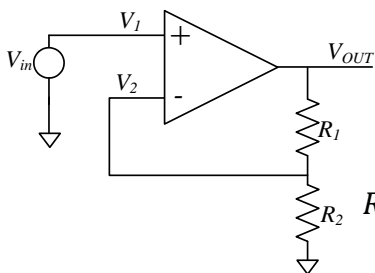
$$R_{in} = R_2 + \frac{R_1 + r_o}{(1 + \beta A)} \approx R_2$$



$$R_{in} = R_d(1 + \beta A)$$

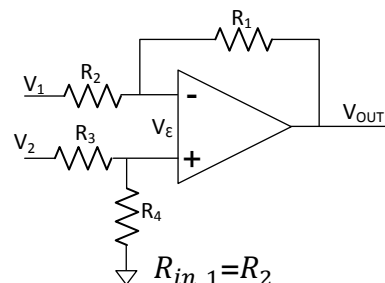

$$\begin{aligned} R_{in_1} &= R_2 \\ R_{in_2} &= R_3 + R_4 \\ R_{in_1,2} &= R_2 + R_3 \end{aligned}$$




Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[15]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Difference Amplifier

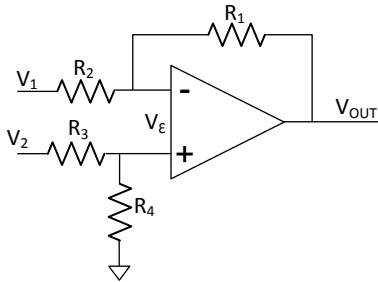


$$V_{out_1} = -V_1 \left(\frac{R_1}{R_2} \right)$$

$$V_{out_2} = V_2 \left(\frac{R_4}{R_3 + R_4} \right) \left(1 + \frac{R_1}{R_2} \right)$$

$$V_{out} = \frac{R_1}{R_2} (V_2 - V_1)$$

$$\frac{R_2}{R_1} = \frac{R_3}{R_4}$$

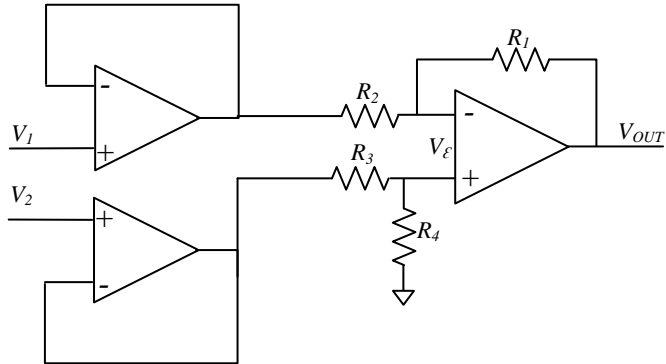

Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[16]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY


Instrumentation Amplifier

$$V_{out} = \frac{R_1}{R_2} (V_{amp_b} - V_{amp_a})$$

$$I_x = \frac{V_1 - V_2}{R_x}$$

$$V_{amp_b} - V_{amp_a} = I_x (R_x + R_a + R_b)$$
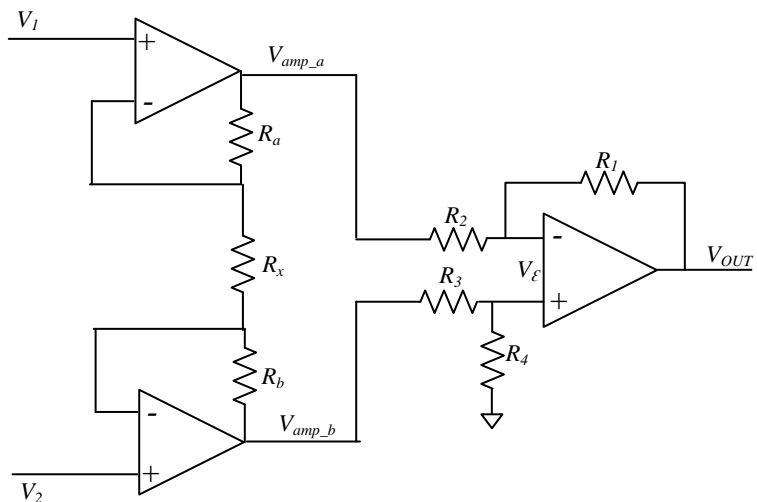
$$V_{out} = \frac{R_1}{R_2} (V_2 - V_1) \left(1 + \frac{R_a + R_b}{R_x} \right)$$







Loop-Gain Nyquist Criterion

$$A_{CL} = G(s) \frac{A_{OL}(s)}{1 + \beta A_{OL}(s)}$$

- The system is unstable if the characteristic equation $\{1 + \beta A_{OL}(s)\}$ has roots in the right half of the complex plane
- Nyquist criterion is a test for location of $\{1 + \beta A_{OL}(s)\}$ roots
- Nyquist criterion can be viewed on the frequency domain (Bode)




Loop-gain on the frequency domain

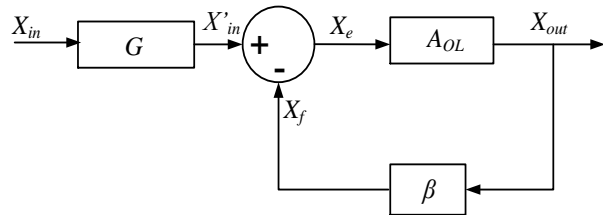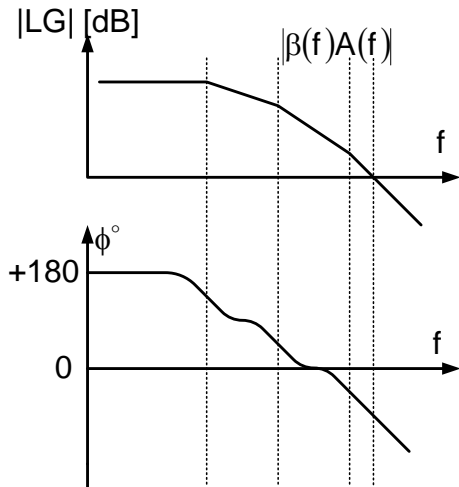

In negative feedback
systems $\phi = 180^\circ (-180^\circ)$
At $f \rightarrow 0$




Bode plot Phase margin

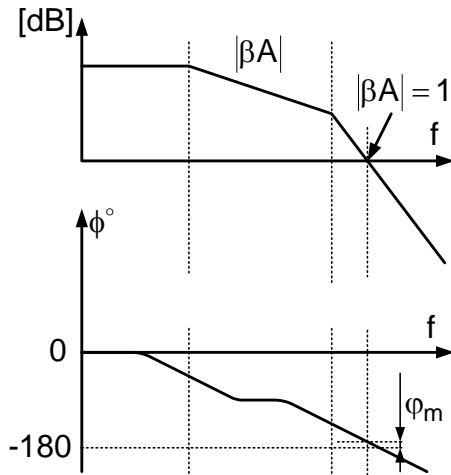

$$\varphi_m = \varphi_{|\beta A|=1} - (-180^\circ) = \varphi_{|\beta A|=1} + 180^\circ$$



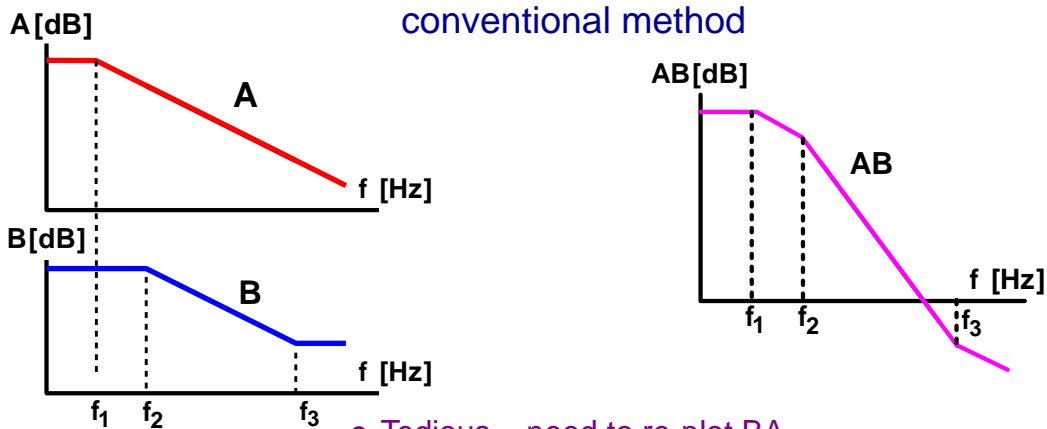
Graphical representation of βA_{OL} conventional method



- Tedious – need to re-plot BA
- Analysis (not design) oriented
- Requires iterations



Graphical Representation of βA_{OL}


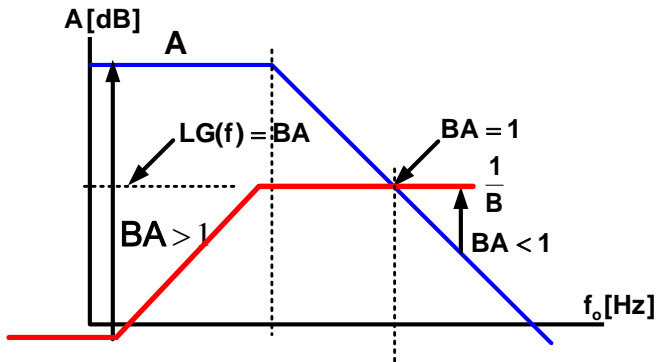


$$20\log A - 20\log \frac{1}{B} = 20\log(BA)$$

$$20\log A = 20\log \frac{1}{B} \Rightarrow B \cdot A = 1$$



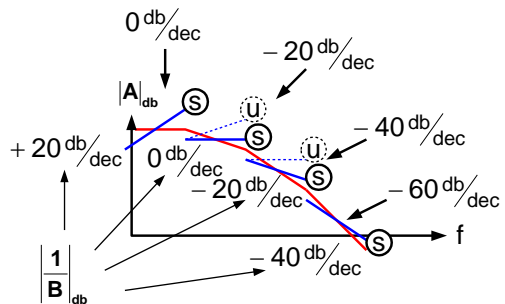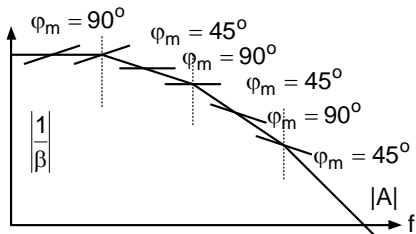Possible compensations Rate of Closure (ROC)






Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671


[23]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

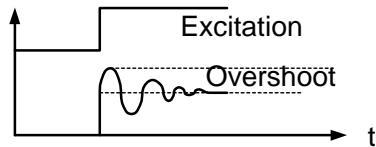
Overshoot and Q in Closed Loop in Response to step in S_{in}


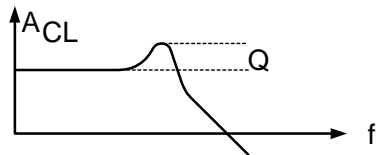
$$Q \cong \frac{\sqrt{\cos\phi_m}}{\sin\phi_m} \quad \text{for } \phi_m < 50^\circ$$



Design target $\phi_m \geq 45^\circ$

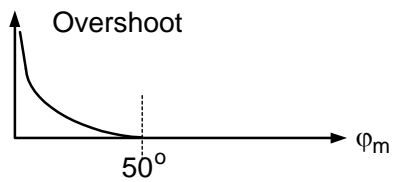


Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[24]

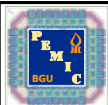THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY



Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[25]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY
