



Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671


[1]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

## Analog Electronic Circuits

Prof. Mor M. Peretz

The Center for Power Electronics and Mixed-Signal IC  
Department of Electrical and Computer Engineering  
Ben-Gurion University of the Negev, *ISRAEL*

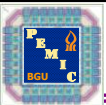Emails: [morp@bgu.ac.il](mailto:morp@bgu.ac.il)Website: <http://www.ee.bgu.ac.il/~pemic>  
<http://www.ee.bgu.ac.il/~analog>

Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[2]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

## Lesson #7 Outline

- Comparators
  - Voltage comparator – basic characteristics
  - Internal circuit
  - Propagation time and overdrive
  - Output stage
- Basic applications
  - Level detection, window, counter, PWM, ON-OFF control
- Schmitt trigger
  - Inverting and noninverting
  - Single supply
- Advanced applications
  - Oscillators





Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[3]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

## Comparator

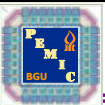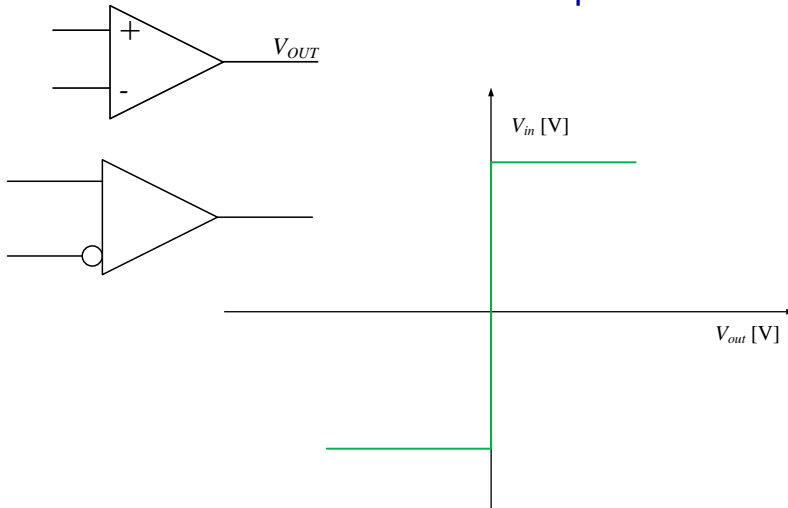


Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[4]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

## Internal circuit

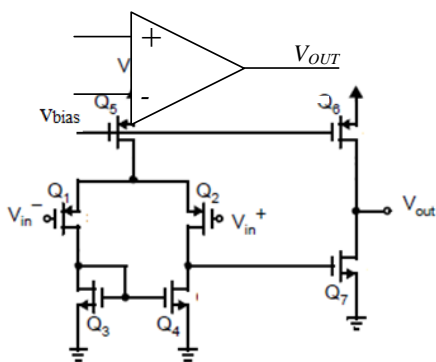

Simple differential



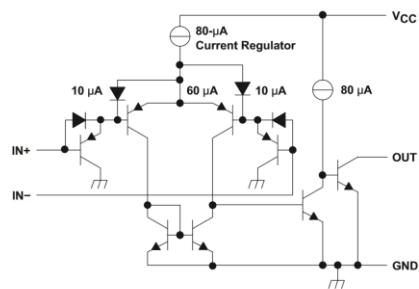


Figure 6. Schematic (Each Comparator)

LM339 (TI)

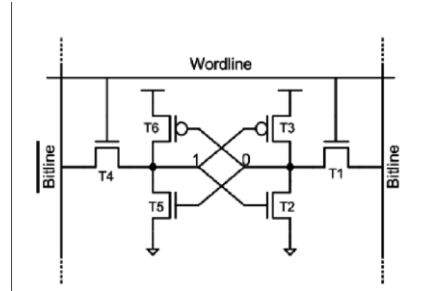



### Internal circuit

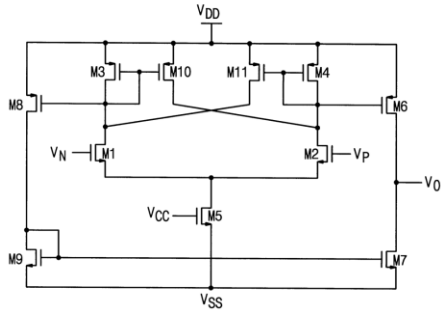

Latched output




### Propagation time and overdrive

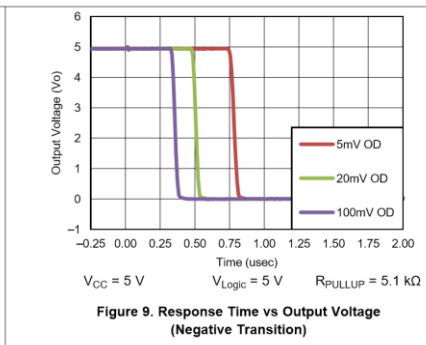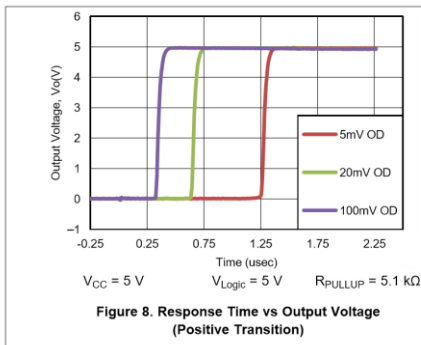



(TI)




### Output stage

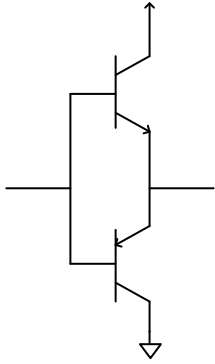

Push-pull



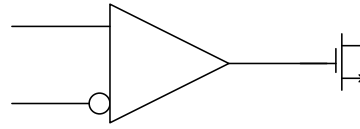
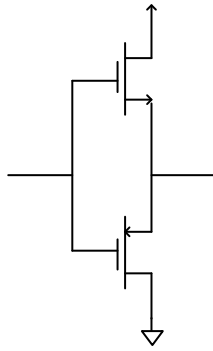


Open-drain  
(Open-Collector)

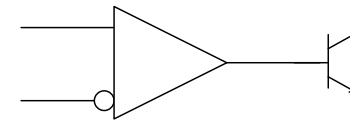
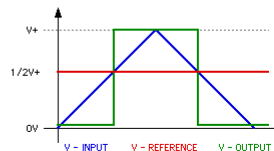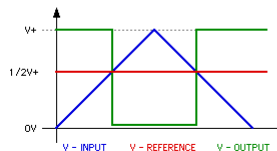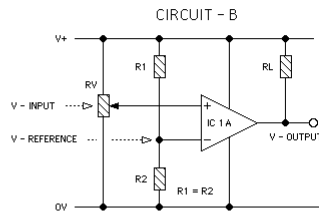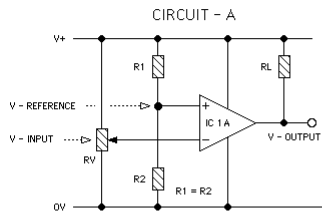
### Basic operation

BASIC OPERATION OF VOLTAGE COMPARATORS  
©ROB PAISLEY 2002  
Comparator Operation



<http://home.cogeco.ca/~rpaisley4/CircuitIndex.html>



Applications –basic

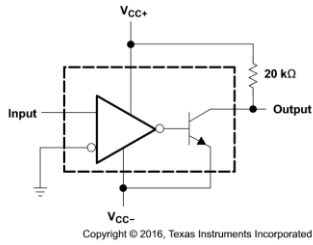


Figure 13. Zero-Crossing Detector


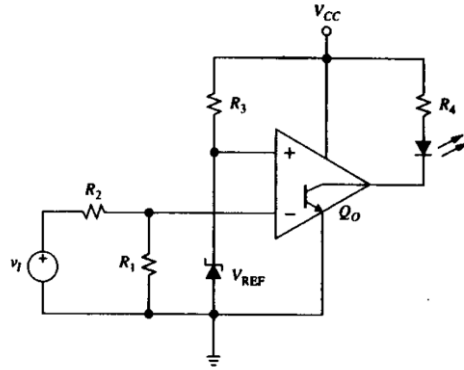


FIGURE 9.11 Basic level detector with optical indicator.

S. Franco

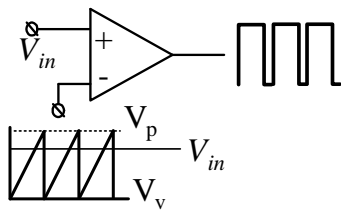

Applications –basic



PWM

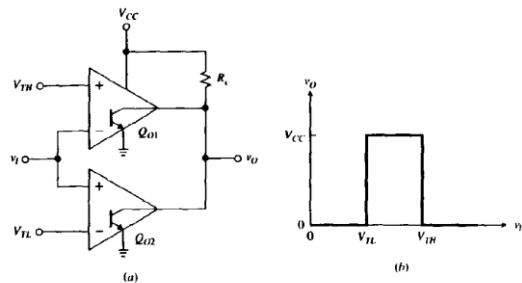


FIGURE 9.13 Window detector and its VTC.

S. Franco



Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[11]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

## Applications –basic


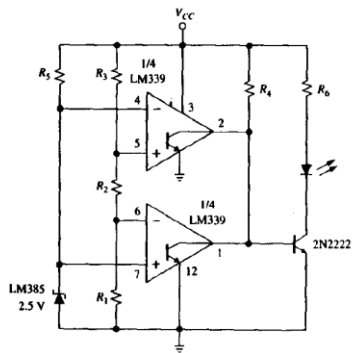
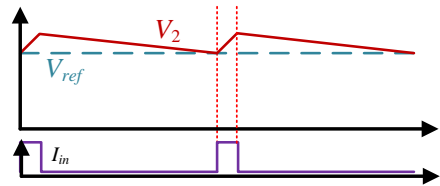


FIGURE 9.14  
Power-supply monitor; LED glows as long as  $V_{CC}$  is within specification.

S. Franco

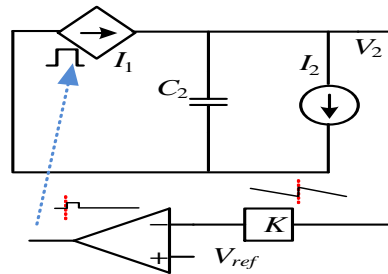


Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[12]

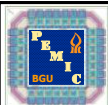THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY



**Prof. Mor M. Peretz**

**Analog Electronic Circuits 361-1-3671**

**[13]**

**THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY**

---