



Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[1]


THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

---

## Analog Electronic Circuits

Prof. Mor M. Peretz

The Center for Power Electronics and Mixed-Signal IC  
Department of Electrical and Computer Engineering  
Ben-Gurion University of the Negev, *ISRAEL*

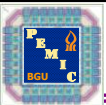Emails: [morp@bgu.ac.il](mailto:morp@bgu.ac.il)Website: <http://www.ee.bgu.ac.il/~pemec>  
<http://www.ee.bgu.ac.il/~analog>

Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[2]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

---

## Lesson #8 Outline

- Rectifiers
  - Rectification basics
  - Precision rectifiers
  - Half-wave
  - Full-wave
- Linear regulation
  - Protection stage
- Datasheet







Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[3]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

## Rectification

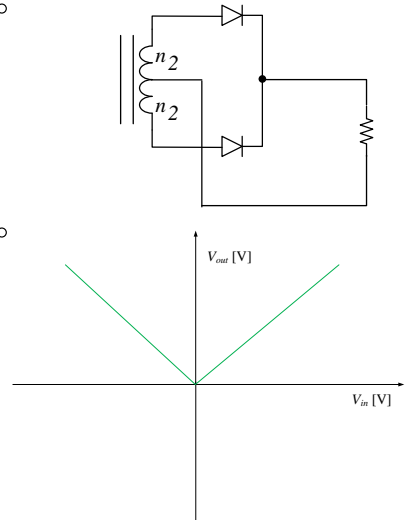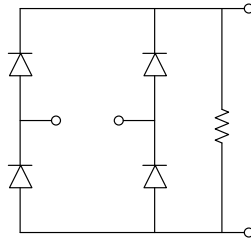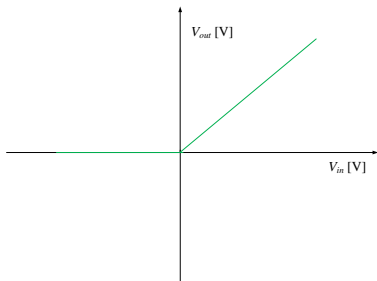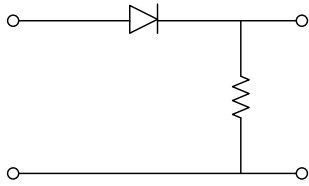


Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671


[4]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

## Half-wave

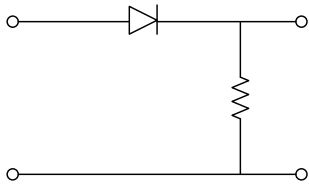

Diode voltage drop

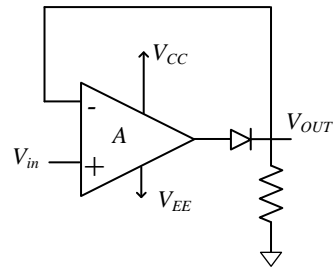

"Super-diode"






Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[5]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

## Half-wave

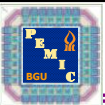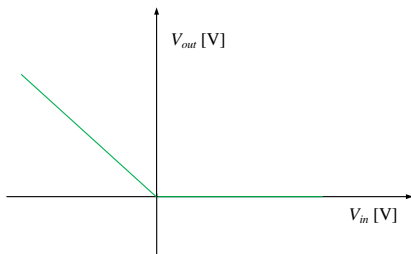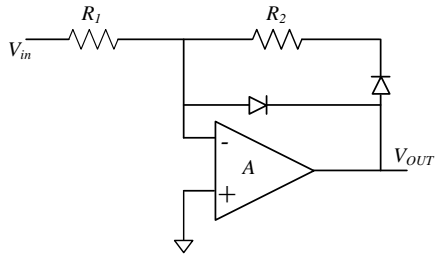





Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[6]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

## Half-wave

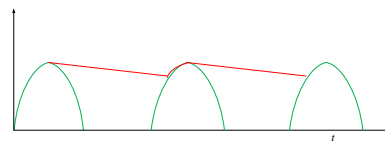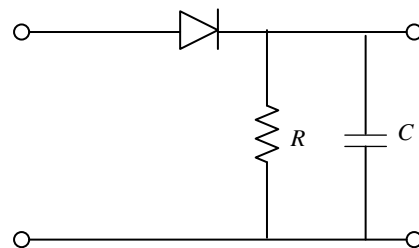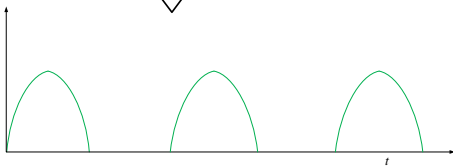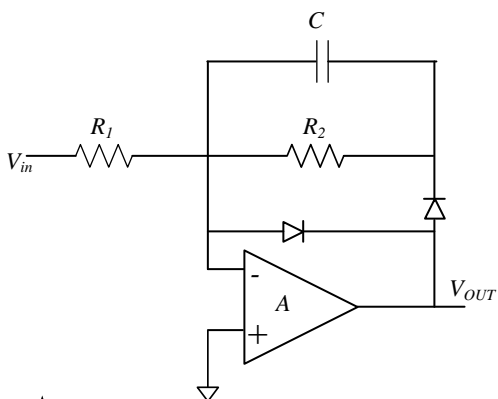




Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[7]

THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

## Half-wave

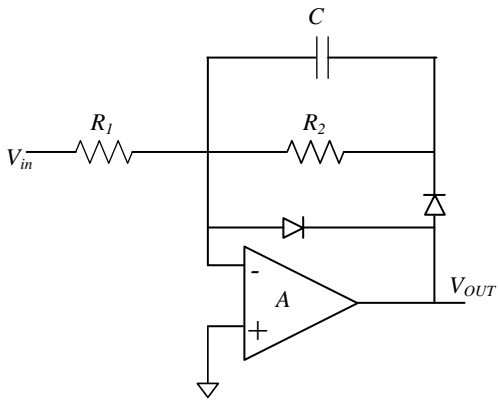

$$I_{av} = \frac{V_{in\_pk}}{R_1} \frac{1}{\pi}$$

$$V_{out} = I_{av} R_2 = \frac{V_{in\_pk}}{R_1} \frac{1}{\pi} R_2$$

$$\Delta V_{out} = \frac{V_{in\_pk}}{R_1} \frac{1}{2\pi f C}$$




Prof. Mor M. Peretz

Analog Electronic Circuits 361-1-3671

[8]


THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

## Full-wave

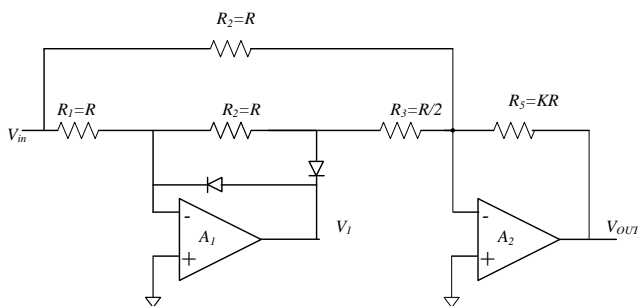



## Linear regulation

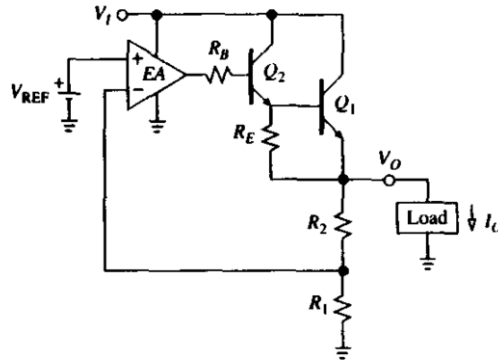


**FIGURE 11.19**  
Basic series voltage regulator.

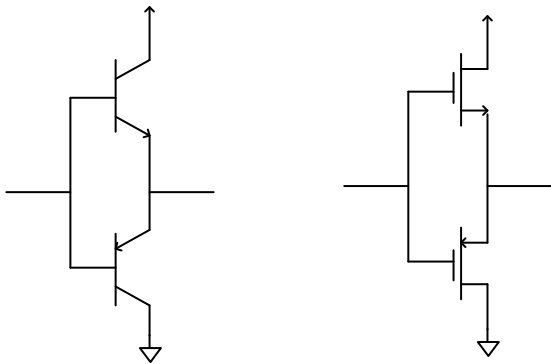S. Franco



## Output stage



Push-pull



### Protection – sourcing current

Schematic Diagram



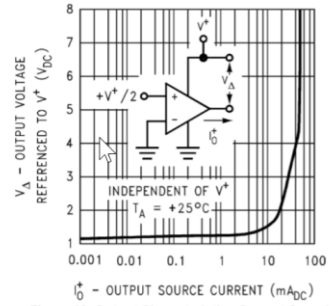
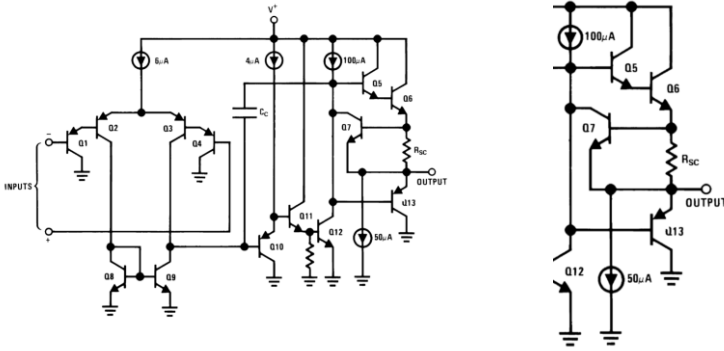


Figure 10. Output Characteristics Current Sourcing


LM324

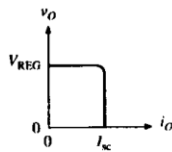

### Protection – sourcing current

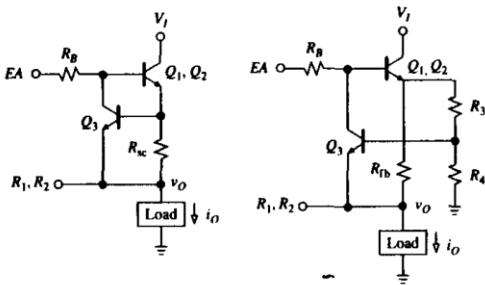

(a)

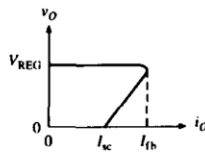


(b)

S. Franco



## Protection – sinking current

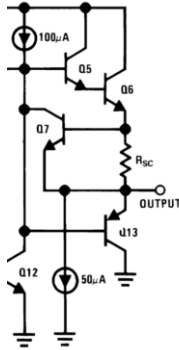

LM324

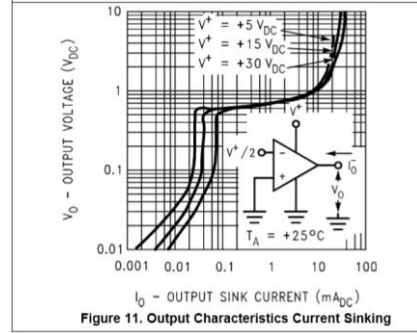


Figure 11. Output Characteristics Current Sinking



LM124-N, LM224-N, LM224-N, LM2902-N, LM324-N

EN53516D - MARCH 2003 - REVISED JANUARY 2011

### LMx24-N, LM2902-N Low-Power, Quad-Operational Amplifiers

#### 1 Features

- Internally Frequency Compensated for Unity Gain
- Large DC Voltage Gain 100 dB
- Wide Bandwidth (Unity Gain) 1 MHz (Temperature Compensated)
- Wide Power Supply Range
  - Single Supply 3 V to 32 V
  - or Dual Supplies ±1.5 V to ±16 V
- Very Low Supply Current Drain (700 µA)
  - Essentially Independent of Supply Voltage
- Low Input Biasing Current 45 nA (Temperature Compensated)
- Low Input Offset Voltage 2 mV and Offset Current 5 nA
- Input Common-Mode Voltage Range Includes Ground
- Differential Input Voltage Range Equal to the Power Supply Voltage
- Large Output Voltage Swing 0 V to V<sup>+</sup> - 1.5 V

#### Advantages:

- Eliminates Need for Dual Supplies
  - Four Internally Compensated Op Amps in a Single Package
  - Allows Direct Sensing Near GND and V<sub>OUT</sub> also Goes to GND
- Compatible With All Forms of Logic
  - Power Drain Suitable for Battery Operation
  - In the Linear Mode the Input Common-Mode Voltage Range Includes Ground and the Output Voltage
  - Can Swing to Ground, Even Though Operated from Only a Single Power Supply Voltage
  - Unity Gain Crossover Frequency is Temperature Compensated
  - Input Bias Current is Also Temperature Compensated

#### 2 Applications

- Transducer Amplifiers
- DC Gain Blocks
- Conventional Op Amp Circuits

#### 3 Description


The LM124-N series consists of four independent, high-gain, internally frequency compensated operational amplifiers designed to operate from a single power supply over a wide range of voltages. Operation from split-power supplies is also possible and the low-power supply current drain is independent of the magnitude of the power supply voltage.

Application areas include transducer amplifiers, DC gain blocks and all the conventional op amp circuits which now can be more easily implemented in single power supply systems. For example, the LM124-N series can directly operate off of the standard 5-V power supply voltage which is used in digital systems and easily provides the required interface electronics without requiring the additional ±15 V power supplies.

Device Information <sup>(1)</sup>		
PART NUMBER	PACKAGE	BODY SIZE (NOM)
LM124-N	CDIP (14)	19.56 mm × 6.67 mm
LM224-N	CDIP (14)	19.56 mm × 6.67 mm
LM324-N	CDIP (14)	19.17 mm × 6.35 mm
	SOIC (14)	8.65 mm × 3.31 mm
	TSSOP (14)	5.00 mm × 4.40 mm
LM2902-N	PDIP (14)	19.17 mm × 6.35 mm
	SOIC (14)	8.65 mm × 3.31 mm
	TSSOP (14)	5.00 mm × 4.40 mm

(1) For all available packages, see the orientable addendum at the end of the datasheet.


#### Schematic Diagram

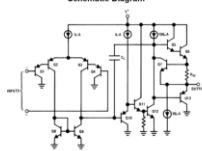

## Datasheet




### 5 Pin Configuration and Functions

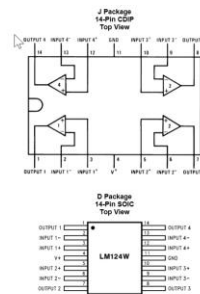

Pin Functions			
PIN	NO.	TYPE	DESCRIPTION
OUTPUT1	1	O	Output, Channel 1
INPUT1-	2	I	Inverting Input, Channel 1
INPUT1+	3	I	Noninverting Input, Channel 1
V+	4	IP	Positive Supply Voltage
INPUT2+	5	I	Noninverting Input, Channel 2
INPUT2-	6	I	Inverting Input, Channel 2
OUTPUT2	7	O	Output, Channel 2
OUTPUT3	8	O	Output, Channel 3
INPUT3-	9	I	Inverting Input, Channel 3
INPUT3+	10	I	Noninverting Input, Channel 3
GND	11	IP	Ground or Negative Supply Voltage
INPUT4+	12	I	Noninverting Input, Channel 4
INPUT4-	13	I	Inverting Input, Channel 4
OUTPUT4	14	O	Output, Channel 4

LM324

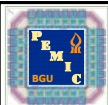

**Prof. Mor M. Peretz**

**Analog Electronic Circuits 361-1-3671**

**[15]**

**THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY**

---



**Prof. Mor M. Peretz**

**Analog Electronic Circuits 361-1-3671**

**[16]**

**THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY**

---