

 Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [1]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Analog Electronic Circuits


Prof. Mor M. Peretz

The Center for Power Electronics and Mixed-Signal IC
 Department of Electrical and Computer Engineering
 Ben-Gurion University of the Negev, ISRAEL
 Emails: morp@bgu.ac.il
 Website: <http://www.ee.bgu.ac.il/~pemic>
<http://www.ee.bgu.ac.il/~analog>

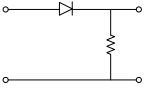

 Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [2]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Lesson #8
Outline


- Rectifiers
 - Rectification basics
 - Precision rectifiers
 - Half-wave
 - Full-wave
- Linear regulation
 - Protection stage
- Datasheet



 Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [3]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY


Rectification




$v_{in}(V)$

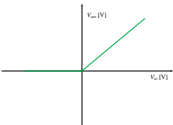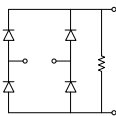



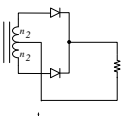


$v_{in}(V)$

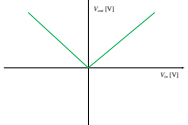


Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [4]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Half-wave

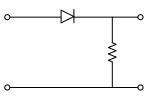


Diode voltage drop

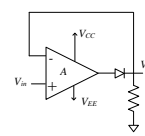


"Super-diode"

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [5]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY


Half-wave

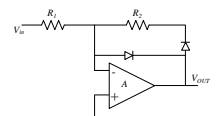



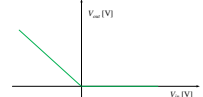


Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [6]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Half-wave

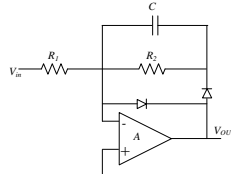

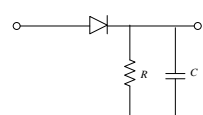

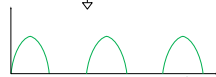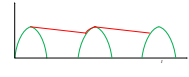Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [7]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Half-wave

$$I_{av} = \frac{V_{in, pk}}{R_1} \frac{1}{\pi}$$

$$V_{out} = I_{av} R_2 = \frac{V_{in, pk}}{R_1} \frac{1}{\pi} R_2$$

$$\Delta V_{out} = \frac{V_{in, pk}}{R_1} \frac{1}{2\pi f C}$$

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [8]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Full-wave

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [9]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Linear regulation

FIGURE 11.19 Basic series voltage regulator.

S. Franco

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [10]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Output stage

Push-pull

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [11]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Protection – sourcing current

Schematic Diagram

LM324

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [12]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Protection – sourcing current

S. Franco