


Exercise 1 solution

Problem 1

$$V_{in} := 10V \quad f_{sw} := 125kHz \quad C := 100\mu F$$

$$D := 0.6 \quad R_L := 15\Omega$$

a) Buck

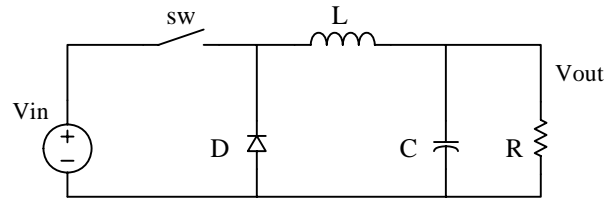

Find inductance L_{min} for CCM:

$$V_o := D \cdot V_{in}$$

$$V_o = 6V$$

$$I_o := \frac{V_o}{R_L}$$

$$I_o = 0.4A$$

Output current equals to inductor average current I_{av} .

Minimum inductance for CCM (more precisely Critical CCM) can be found the following way:

$$\Delta I = 2 \cdot I_{av} = 2 \cdot I_o \quad \Delta I = \frac{(V_{in} - V_o) \cdot D}{L \cdot f_{sw}}$$

$$L_{min} := \frac{(V_{in} - V_o) \cdot D}{2 \cdot I_o \cdot f_{sw}}$$

$$L_{min} = 24 \cdot \mu H$$

$$L := 5 \cdot L_{min}$$

$$L = 120 \cdot \mu H$$

$$P_o := V_o \cdot I_o$$

$$P_o = 2.4W$$

$$\Delta I := \frac{(V_{in} - V_o) \cdot D}{L \cdot f_{sw}}$$

$$\Delta I = 0.16A$$

$$I_{L_{av}} := I_o$$

$$I_{L_{av}} = 0.4A$$

$$I_{D_{av}} := I_o \cdot (1 - D)$$

$$I_{D_{av}} = 0.16A$$

For triangular waveform the RMS current :

$$I_{L_{rms}} := \sqrt{\left(I_{L_{av}} - \frac{\Delta I}{2}\right) \cdot \left(I_{L_{av}} + \frac{\Delta I}{2}\right) + \frac{\Delta I^2}{3}}$$

$$I_{L_{rms}} = 0.403A$$


$$I_{L_{rms2}} := \sqrt{I_{L_{av}}^2 + \frac{\left(\frac{\Delta I}{2}\right)^2}{3}}$$

$$I_{L_{rms2}} = 0.403A$$

$$V_{D_{max}} = V_{in}$$

$$V_{SW_{max}} = V_{in}$$

b) Boost

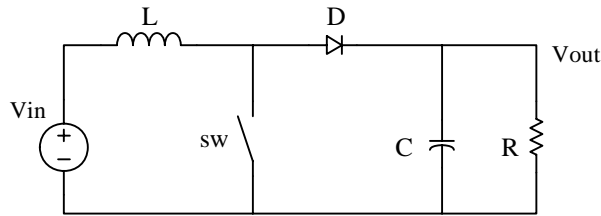

Find inductance L_{\min} for CCM:

$$V_o := V_{in} \cdot \frac{1}{1 - D}$$

$$V_o = 25 \text{ V}$$

$$I_o := \frac{V_o}{R_L}$$


$$I_o = 1.667 \text{ A}$$

Output current equals to diode average current $I_{D_{av}}$.

Minimum inductance for CCM can be found the following way:

$$\Delta I = 2 \cdot I_D = \frac{2 \cdot I_o}{1 - D}$$
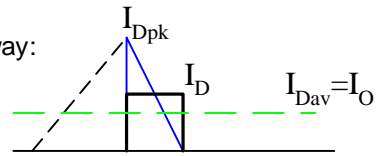
$$\Delta I = \frac{V_{in} \cdot D}{L \cdot f_{sw}}$$



$$L_{\min} := \frac{V_{in} \cdot D \cdot (1 - D)}{2 \cdot I_o \cdot f_{sw}}$$

$$L_{\min} = 5.76 \cdot \mu\text{H}$$

$$L := 5 \cdot L_{\min}$$

$$L = 28.8 \cdot \mu\text{H}$$

$$P_o := V_o \cdot I_o$$

$$P_o = 41.667 \text{ W}$$

$$\Delta I := \frac{V_{in} \cdot D}{L \cdot f_{sw}}$$

$$\Delta I = 1.667 \text{ A}$$

$$I_{L_{av}} := \frac{I_o}{1 - D}$$

$$I_{L_{av}} = 4.167 \text{ A}$$

$$I_{D_{av}} := I_o$$

$$I_{D_{av}} = 1.667 \text{ A}$$

For triangular waveform the RMS current :

$$I_{L_{rms}} := \sqrt{\left(I_{L_{av}} - \frac{\Delta I}{2}\right) \cdot \left(I_{L_{av}} + \frac{\Delta I}{2}\right) + \frac{\Delta I^2}{3}}$$


$$I_{L_{rms}} = 4.194 \text{ A}$$

$$V_{D_{max}} = V_o$$

$$V_{SW_{max}} = V_o$$

Problem 2

Buck converter:

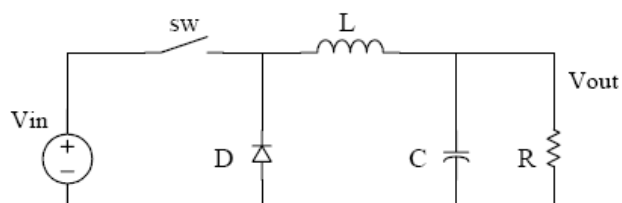

Current waveform for Discontinuous Mode:

For the steady state operation the average current through the inductor L is constant and average voltage equals zero.

$$(V_{in} - V_o) \cdot D_{on} = V_o \cdot D_f \quad D_f \text{ is discharge part of the period.}$$

$$\frac{V_o \cdot D_{on}}{V_{in} \cdot D_{on} + D_f} \quad (\text{When } D_f = 1 - D_{on} \text{ we have "regular" formula for Buck converter})$$

$$\Delta I = \frac{V_o \cdot D_f}{L \cdot f_{sw}} \Rightarrow D_f = \frac{L \cdot f_{sw} \cdot \Delta I}{V_o}$$

Output current equals to the average inductor current:

$$I_o = I_{L_{av}} = \frac{\Delta I}{2} \cdot (D_{on} + D_f) = \frac{V_o}{R_L} \quad R_L - \text{load resistance}$$

$$\Delta I = \frac{2 V_o}{R_L} \cdot \frac{1}{(D_{on} + D_f)}$$

$$D_f = \frac{L \cdot f_{sw} \cdot 2}{R_L \cdot (D_{on} + D_f)}$$


$$D_f^2 + D_{on} \cdot D_f - \frac{2L \cdot f_{sw}}{R_L} = 0$$

Solving this equation we can find D_f :

$$D_f = \sqrt{\frac{D_{on}^2}{4} + 2 \cdot \frac{L \cdot f_{sw}}{R_L}} - \frac{D_{on}}{2}$$

$$\frac{V_o}{V_{in}} = \frac{D_{on}}{D_{on} + \sqrt{\frac{D_{on}^2}{4} + 2 \cdot \frac{L \cdot f_{sw}}{R_L}}} = \frac{D_{on}}{\frac{D_{on}}{2} + \sqrt{\frac{D_{on}^2}{4} + 2 \cdot \frac{L \cdot f_{sw}}{R_L}}}$$

Boost converter:

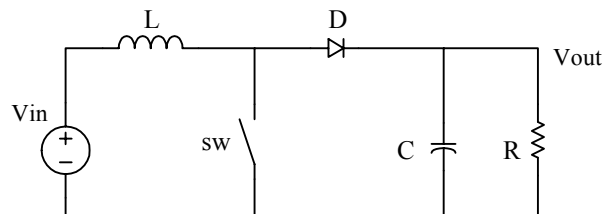

Average voltage on the inductor L is zero:

$$V_{in} \cdot D_{on} = (V_o - V_{in}) \cdot D_f$$

Input power equals to the output power (supposing the losses are negligible).

$$P_{in} = V_{in} \cdot I_{in_{av}} = P_{out} = \frac{V_o^2}{R_L}$$

$$I_{in_{av}} = \frac{\Delta I}{2} \cdot (D_{on} + D_f)$$

$$\Delta I = \frac{V_{in} \cdot D_{on}}{L \cdot f_{sw}}$$


$$P_{in} = V_{in} \cdot \frac{V_{in} \cdot D_{on}}{2 \cdot L \cdot f_{sw}} \cdot (D_{on} + D_f)$$

$$\left| \begin{array}{l} \frac{V_{in}^2 \cdot D_{on}}{2 \cdot L \cdot f_{sw}} \cdot (D_{on} + D_f) = \frac{V_o^2}{R_L} \\ V_{in} \cdot D_{on} = (V_o - V_{in}) \cdot D_f \end{array} \right.$$

Solving the previous set of two equations for V_o , we have:

$$\frac{V_o}{V_{in}} = \frac{1}{2} \cdot \left(1 + \sqrt{1 + \frac{2 \cdot D_{on}^2 \cdot R_L}{L \cdot f_{sw}}} \right)$$

Flyback converter:

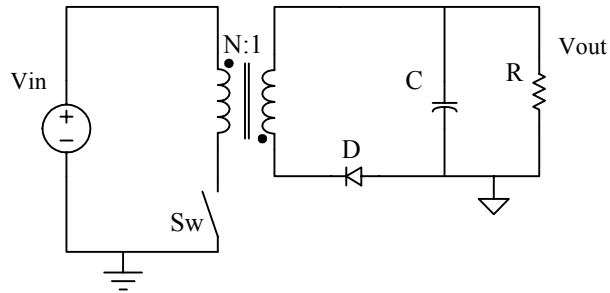

Average voltage on the inductor L is zero:

$$V_{in} \cdot D_{on} = V_o \cdot N \cdot D_f$$

$$P_{out} = \frac{V_o^2}{R_L} = \frac{\Delta I_s^2 \cdot L_s}{2} \cdot f_{sw}$$

$$\Delta I_s = \frac{V_o \cdot D_f}{L_s \cdot f_{sw}}$$

$$\frac{V_o^2}{R_L} = \left(\frac{V_o \cdot D_f}{L_s \cdot f_{sw}} \right)^2 \cdot \frac{L_s}{2} \cdot f_{sw} \quad \Rightarrow \quad D_f^2 = \frac{2 L_s \cdot f_{sw}}{R_L}$$


Substituting in the first equation:

$$V_{in} \cdot D_{on} = V_o \cdot N \cdot \sqrt{\frac{2 L_s \cdot f_{sw}}{R_L}} = V_o \cdot N \cdot \sqrt{\frac{2 L \cdot f_{sw}}{R_L \cdot N^2}}$$

$$\frac{V_o}{V_{in}} = D_{on} \cdot \sqrt{\frac{R_L}{2 L \cdot f_{sw}}}$$

Problem 3:

Tapped boost converter:

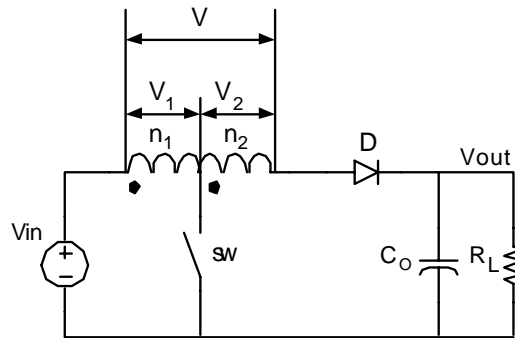

$$\frac{V}{n} = \frac{d\phi}{dt}$$

Since the magnetic flux must maintain continuous, we obtain:


$$\frac{V}{n_1 + n_2} = \frac{V_1}{n_1} \quad \text{-----} \quad \frac{V}{V_1} = \frac{n_1 + n_2}{n_1} = n$$

Separate the operation into two sub-intervals: ON and OFF

ON sub-interval:


$$V_1 = V_{in}$$
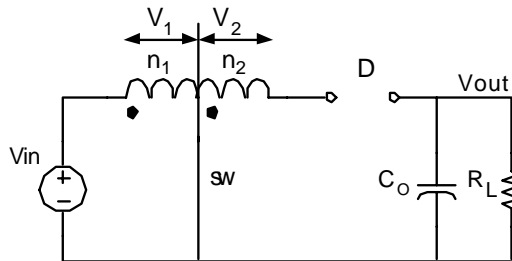
$$V = V_{in} \left(\frac{n_1 + n_2}{n_1} \right)$$



OFF sub-interval:

$$V = V_{in} - V_{out}$$

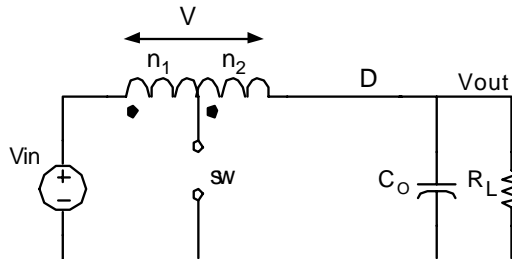

The average voltage <V> of the inductor L must be zero for every switching cycle.

$$V_{in} \cdot D \left(\frac{n_1 + n_2}{n_1} \right) + (V_{in} - V_{out})(1 - D) = 0$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 - D} \cdot \left(1 + D \cdot \frac{n_2}{n_1} \right)$$

