



DC-DC Converters

Dr. Mor M. Peretz

Power Electronics Laboratory
Department of Electrical and Computer Engineering
Ben-Gurion University of the Negev, ISRAEL
Emails: morp@ee.bgu.ac.il ; dcdc@ee.bgu.ac.il
Website: <http://www.ee.bgu.ac.il/~dcdc>

© All rights reserved. Duplication or copying is not permitted
without written permission by author



Background and Scope

- Analog Electronics
- Power Electronics
- Provides knowledge and tools for analysis and design of Switch-Mode Power Systems (SMPS)

- PWM Converters
- Magnetics
- Passive and active elements
- Control

Introductory Course



Course Information

- Lectures
- HW assignments
- Laboratory – Mandatory

- Grading: Final Exam – 75%, Lab – 25%


- Office Hours:

- Website: <http://www.ee.bgu.ac.il/~dcdc>




Power Conversion

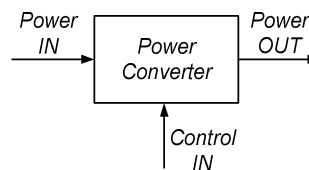- AC-DC (Rectifier)
- DC-DC (Converter)
- DC-AC (Inverter)
- AC-AC (Cyclo-converter)






Linear regulators

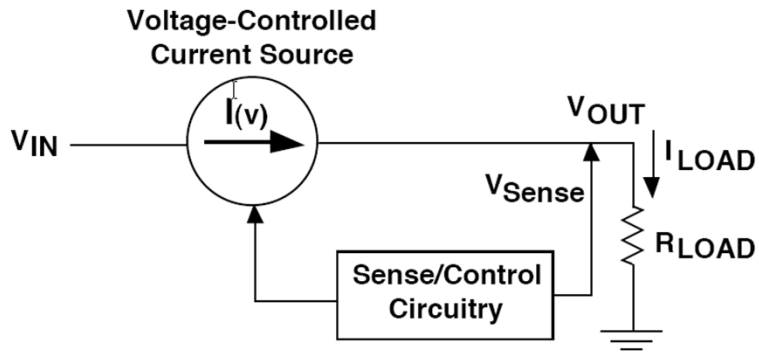

The problem of linear regulation Example

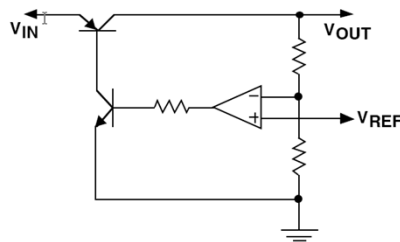

- $V_{in} = 10V$
- $V_{out} = 5V$
- $I_{out} = 5A$
- Efficiency: 50%
- Power loss: 25W (Heat dissipation)



Switch-mode converters



- Reactive elements
- on/off switches

Advantages:

- High efficiency
- Small size

Disadvantages:


- Reliability
- Cost
- Noise

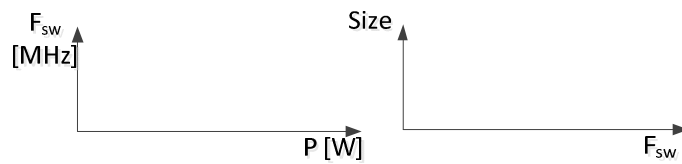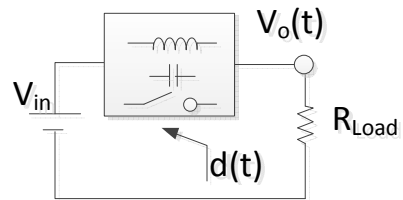


PWM converters

Inductor

$$\frac{V}{L} = \frac{di}{dt}$$

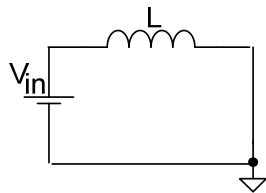


PWM converters Inductor

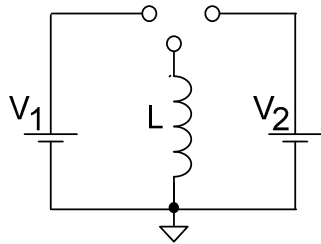

$$\frac{V}{L} = \frac{di}{dt}$$

PWM converters Inductor

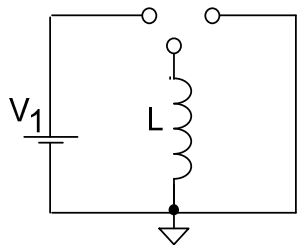


$$\frac{V}{L} = \frac{di}{dt}$$



PWM converters Inductor average voltage

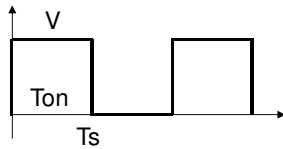Still valid: $\frac{\bar{V}}{L} = \frac{d \bar{I}}{dt}$




The average voltage across the inductor must be zero

$$\bar{V}_L = 0$$

Why???



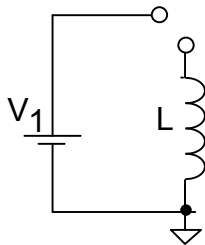
PWM converters Inductor Current Interruption



Polarity at the interruption instance: Imaginary resistor method



Operation of Buck converter

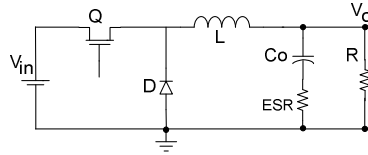


On

Waveforms

Off




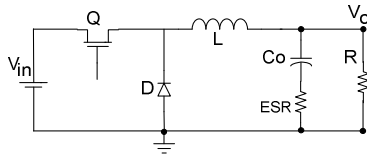Operation of Buck converter Voltage transfer function – CCM ΔI method







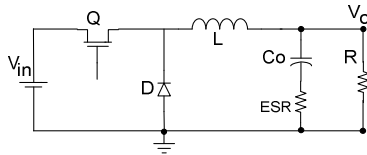Operation of Buck converter Voltage transfer function – CCM average voltage method




Operation of Buck converter DCM

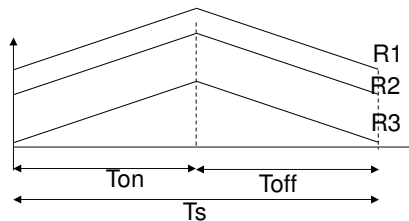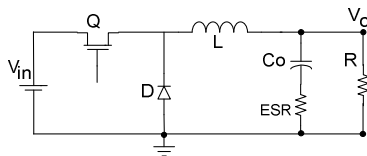

$R1 < R2 < R3$



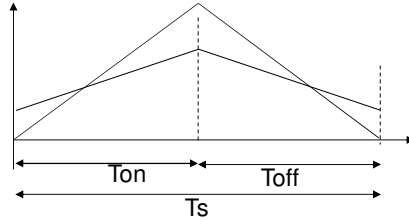Operation of Buck converter Boundary mode - Lmin





$$I_{pk} = \frac{V_o}{L_{min}} T_{off} = 2I_{av}$$

$$L_{min} = \frac{V_o D_{off}}{2I_{av} f_s}$$



Operation of Buck converter DCM

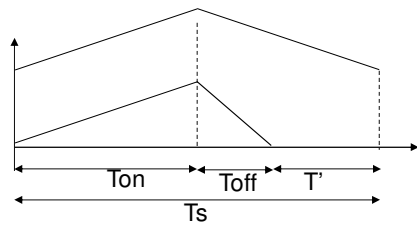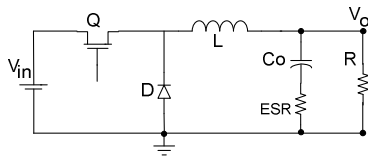

$$I_{pk} = \frac{V_{in} - V_o}{L} T_{on} = \frac{V_o}{L} T_{off}'$$


$$D_{off}' = \frac{V_{in} - V_o}{V_o} D_{on}$$

$$I_{av} = \frac{1}{T_s} \left(\frac{I_{pk}(T_{on} + T_{off}')}{2} \right) = \frac{V_o}{R}$$


$$\frac{V_o}{V_{in}} = \frac{R D_{on}^2 T_s}{4L} \left(\sqrt{1 + \frac{8L}{R D_{on}^2 T_s}} - 1 \right)$$



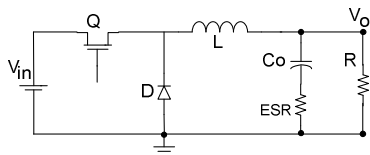Operation of Buck converter Output capacitor



ΔV_o is small

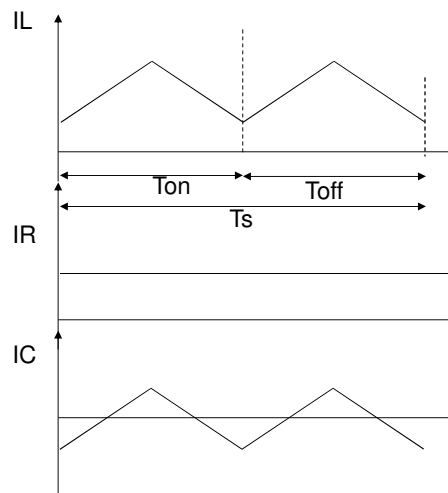


Buck converter Design Example

- $V_{in} = 10\text{v}$; $V_{out} = 5\text{V}$; $I_{out} = 5\text{A}$; $f_s = 100\text{kHz}$
- Calculate L_{min}



Operation of Boost converter

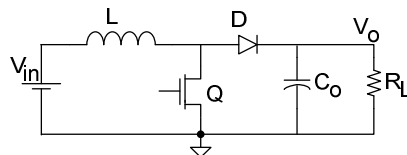


On

Waveforms

Off




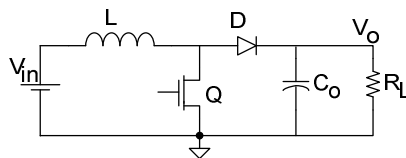Operation of Boost converter Voltage transfer function – CCM ΔI method






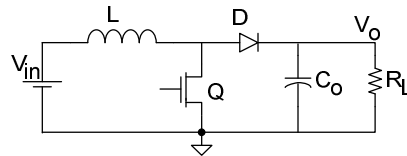Operation of Boost converter Voltage transfer function – CCM average voltage method



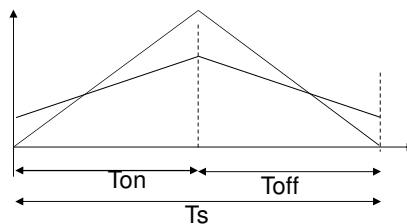Operation of Boost converter Boundary mode - L_{min}





$$I_{pk} = \frac{V_{in}}{L_{min}} T_{on} = 2I_{av}$$

$$L_{min} = \frac{V_{in} D_{on}}{2I_{av} f_s}$$



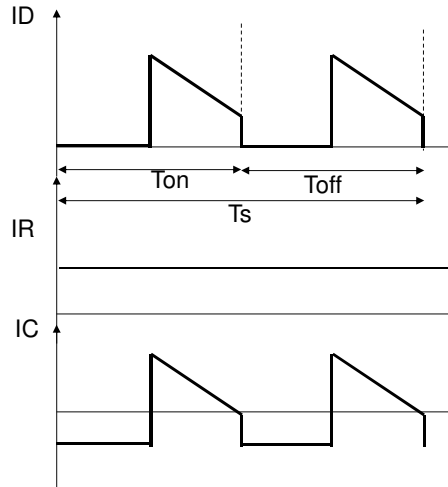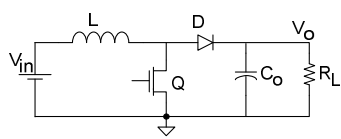Operation of Boost converter Output capacitor



ΔV_o is small




Boost converter Design Example

- $V_{in} = 12V$; $V_{out} = 48V$; $I_{out} = 1A$; $f_s = 50kHz$
- Calculate L for $\Delta I = 0.1 I_{Lavg}$



Operation of Buck-Boost converter

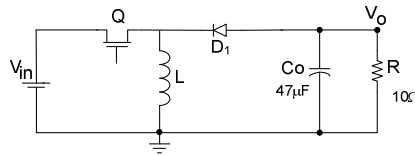


On

Waveforms

Off




Types of PWM converters Basic

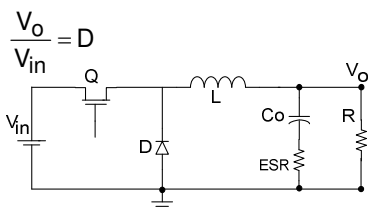


Buck

$$\frac{V_o}{V_{in}} = D$$

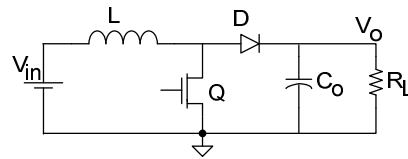

Boost

$$\frac{V_o}{V_{in}} = \frac{1}{1-D}$$

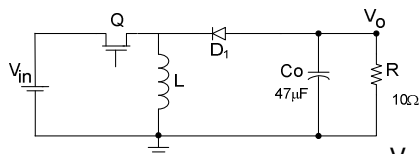

Buck-Boost


$$\frac{V_o}{V_{in}} = -\frac{D}{1-D}$$



Input and Output Currents




Simulation

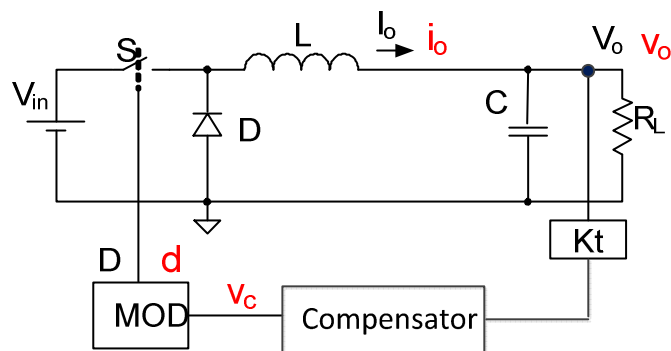


- Cycle-by-cycle Vs. Average simulation
- Objective: Create a continuous model



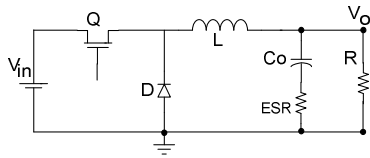
Average Simulation Common Switched-Inductor Cell



Buck

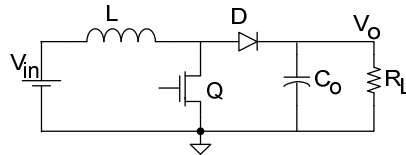



Boost

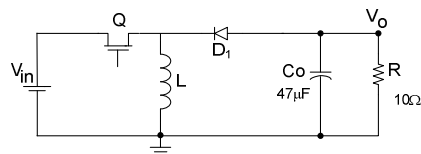

Buck-Boost



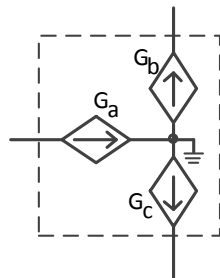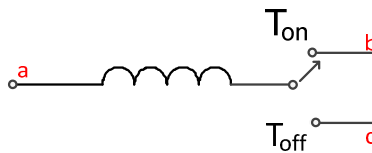Switched Inductor Model (SIM) Continuous model




$$I_a = I_L$$


$$I_b = I_L D_{on}$$

$$I_c = I_L D_{off}$$

The SIM with Average Current

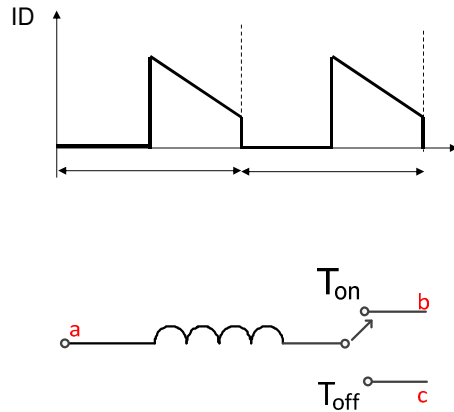


Auxiliary Circuit to Create IL

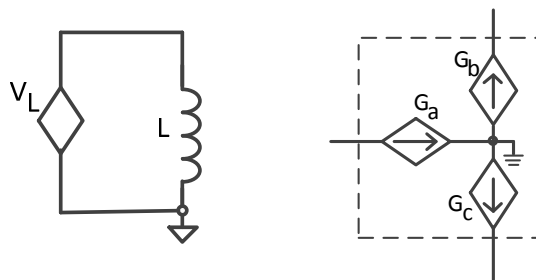


$$\overline{V}_L = \frac{V(a,b)T_{on} + V(a,c)T_{off}}{T_s}$$




Complete Average Model

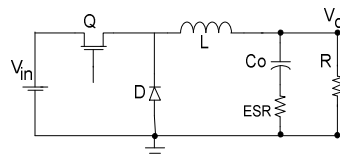

Formal method

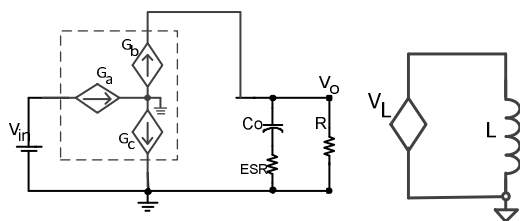


Complete Average Model By inspection

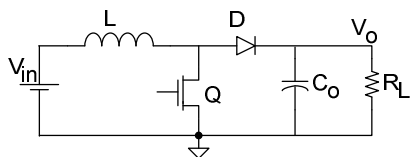



Complete Average Model By inspection

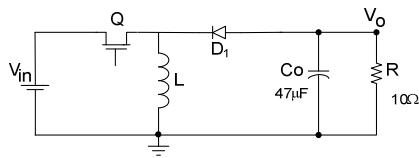

In the Simulator Environment Coding variables into voltages





