

Mor M. Peretz, Switch-Mode Power Supplies [8-1]

Control of switch-mode converters

Mor M. Peretz, Switch-Mode Power Supplies [8-2]

Control objectives

Produce control command to

- Regulate the output voltage
- Obtain zero or small steady-state (DC) error
- Quick response to reference changes
- Fast recovery
- Immunity to input and load changes
- Reasonable overshoot

Mor M. Peretz, Switch-Mode Power Supplies [8-3]

Switch-mode converters as feedback systems

$\frac{v_o}{d}(f)$ Power stage $\frac{v_e}{v_o}(f)$ Compensator $\frac{d}{v_e}(f)$ Modulator

- Power stage is a Switching System (non-linear)
- Compensator is an analog or digital controller
- Linear control theory based design → small signal response

Mor M. Peretz, Switch-Mode Power Supplies [8-4]

Control of PWM converters disturbances in voltage mode

Mor M. Peretz, Switch-Mode Power Supplies [8-5]

Voltage regulation

Mor M. Peretz, Switch-Mode Power Supplies [8-6]

PWM modulator

$$V_i = \frac{(V_p - V_v)t}{T_s} + V_v$$

$$V_i = V_c = \frac{(V_p - V_v)t_{on}}{T_s} + V_v$$

$$\frac{t_{on}}{T_s} = D_{on} = \frac{(V_c - V_v)}{V_p - V_v}$$

Practical $D_{on\ max} \approx 0.8 \div 0.9$

Mor M. Peretz, Switch-Mode Power Supplies [8-7]

Sawtooth generator

Mor M. Peretz, Switch-Mode Power Supplies [8-8]

Transfer functions

Mor M. Peretz, Switch-Mode Power Supplies [8-9]

Control of PWM converters disturbances in voltage mode

$$A_d = \frac{v_{out}}{d} \Big|_{v_{in}=0, i_{out}=0}$$

$$A_{vin} = \frac{v_{out}}{v_{in}} \Big|_{d=0, i_{out}=0}$$

$$Z_{out} = \frac{v_{out}}{i_{out}} \Big|_{v_{in}=0, d=0}$$

$$v_{out} = dA_d + v_{in}A_{vin} - i_{out}Z_{out}$$

$$v_{out} = v_{ref} \frac{1}{K_t} \frac{LG}{1+LG} + v_{in} \frac{A_{vin}}{1+LG} - i_{out} \frac{Z_{out}}{1+LG}$$

$LG = K_t K_M B A_d$

Mor M. Peretz, Switch-Mode Power Supplies [8-10]

Dynamics of feedback systems

Block diagram division

$LG(f) = AB$

A – known (power stage + divider)
 B – unknown (have to be designed)

Mor M. Peretz, Switch-Mode Power Supplies [8-11]

LoopGain test

Nyquist Criterion


$$A_{CL} = \frac{A(s)}{1+LG(s)}$$


- The system is unstable if $\{1+LG(s)\}$ has roots in the right half of the complex plane.
- Nyquist criterion is a test for location of $\{1+LG(s)\}$ roots.
- Nyquist criterion is normally translated into the Bode plane (frequency domain)


Mor M. Peretz, Switch-Mode Power Supplies [8-12]


LoopGain test

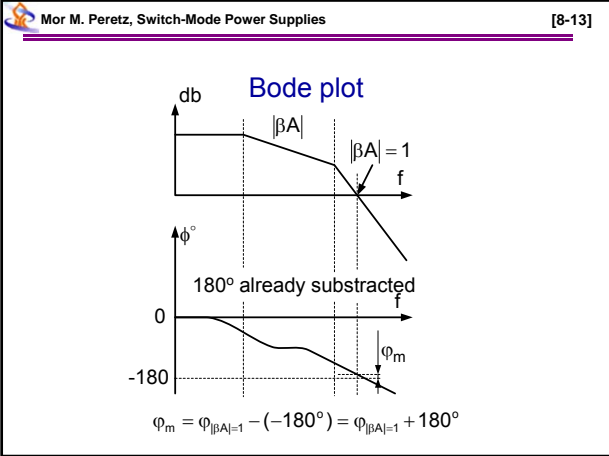
In negative feedback systems $\phi = 180^\circ (-180^\circ)$
 At $f \rightarrow 0$




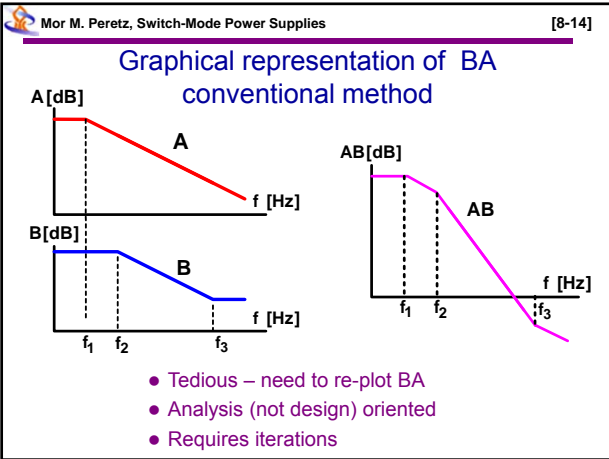

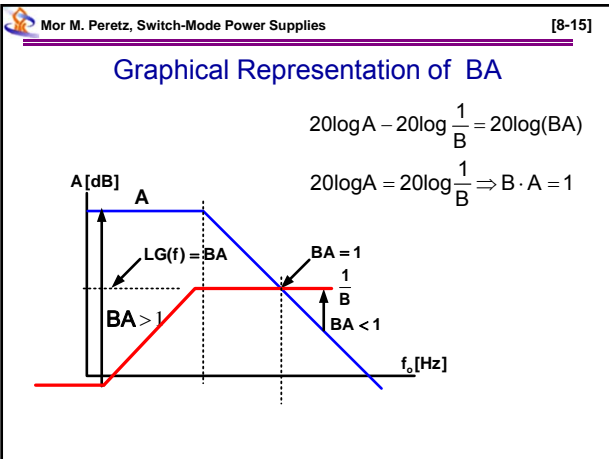

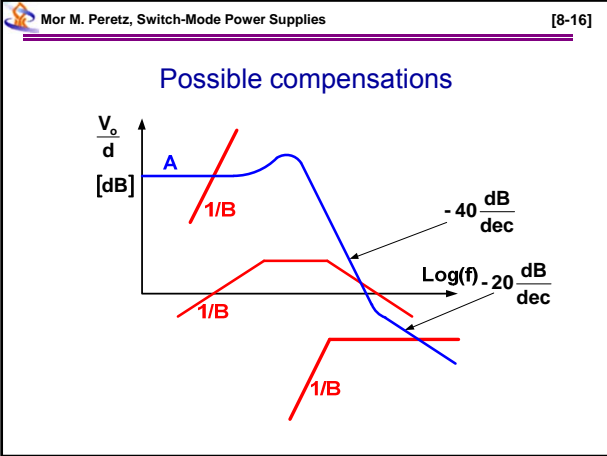

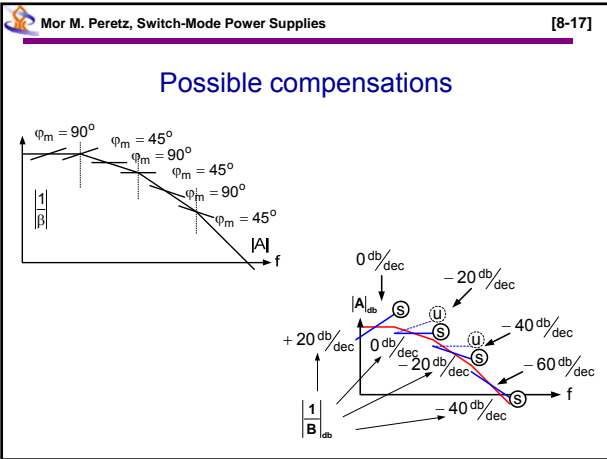

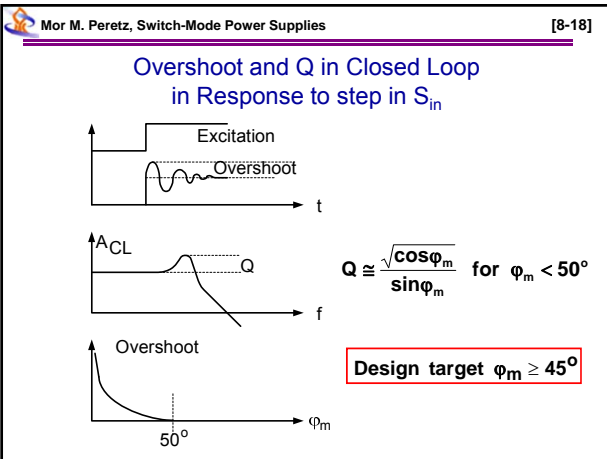

Mor M. Peretz, Switch-Mode Power Supplies [8-19]

Extracting the power stage control-to-output transfer function

The diagram shows a buck converter circuit with input voltage V_{in} , switch S , diode D , inductor L , capacitor C_o , and load resistor R_o . The output voltage is V_o . Below it, the equivalent circuit for control-to-output transfer function extraction is shown, featuring a dependent current source G_b and a dependent voltage source E_{in} in series with the inductor L , capacitor C_o , and load resistor R_o .

$E_{in} = V_{in} \cdot D_{in}$
 $G_b = \bar{I}_L \cdot D_{in}$
 $E_{in} - V_o \rightarrow \bar{V}_L$

Mor M. Peretz, Switch-Mode Power Supplies [8-20]

Linearization

The diagram shows a dependent voltage source $V(in) I(3)$ in series with a resistor R . The output voltage is $V(out)$.

$V(out) = V(in) * I(3)$

$$d(V(out)) = \frac{\partial(V(out))}{\partial(V(in))} v(in) + \frac{\partial(V(out))}{\partial(I(3))} i(3)$$

$$V(out) = \frac{\Delta V(out)}{\Delta V(in)} v(in) + \frac{\Delta V(out)}{\Delta I(3)} i(3)$$

Mor M. Peretz, Switch-Mode Power Supplies [8-21]

SPICE Linearization (AC Analysis)

The diagram shows two dependent sources in series with a resistor R . The first is a dependent voltage source $V(in) I(3)$. The second is a dependent voltage source $\left[\frac{\Delta F}{\Delta I(3)} \right]_o \cdot i(3)$. The output voltage is $V(out)$.

$\frac{\Delta F}{\Delta V(in)} = I(3)_o$
 $\frac{\Delta F}{\Delta I(3)} = V(in)_o$

Mor M. Peretz, Switch-Mode Power Supplies [8-22]

Buck linearization

$E_{in} = V_{in}D$
 $G_b = \bar{I}_L D$

$\left[\frac{\Delta E_{in}}{\Delta D} \right]_o$
 $\left[\frac{\Delta G_b}{\Delta D} \right]_o$
 $\left[\frac{\Delta E_{in}}{\Delta \bar{I}_L} \right]_o$
 $\left[\frac{\Delta V_{in}}{\Delta \bar{I}_L} \right]_o$

Mor M. Peretz, Switch-Mode Power Supplies [8-23]

Possible phase compensation schemes


Lag network


$A_o = \frac{R_f}{R_{in}}$


$f_p = \frac{1}{2\pi C_f R_f}$
 one pole


Mor M. Peretz, Switch-Mode Power Supplies [8-24]


Design example

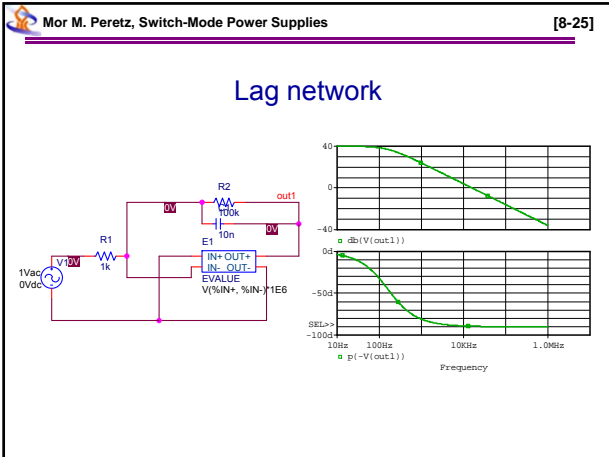


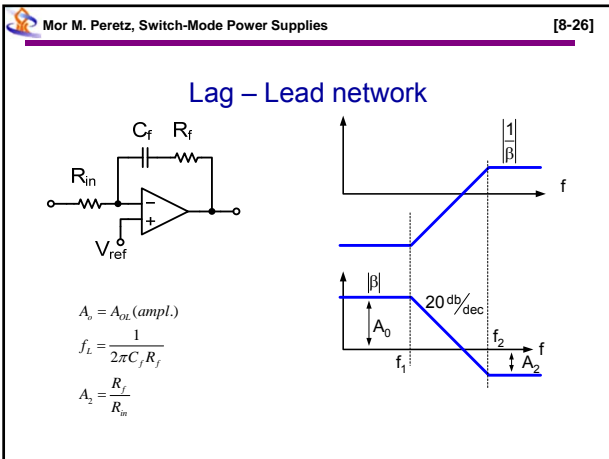

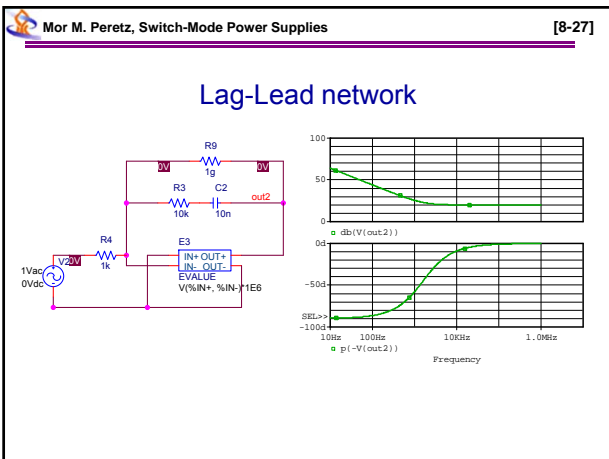

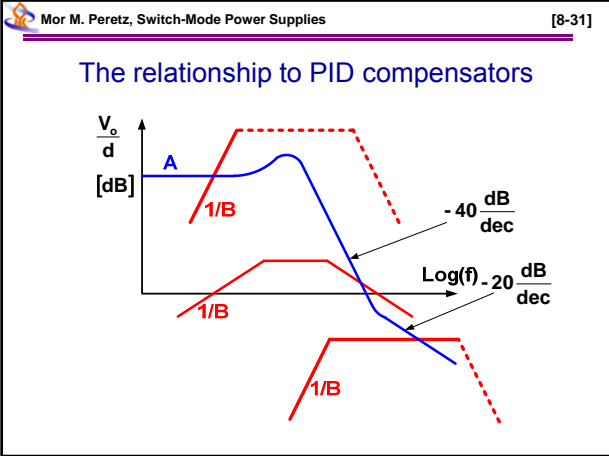

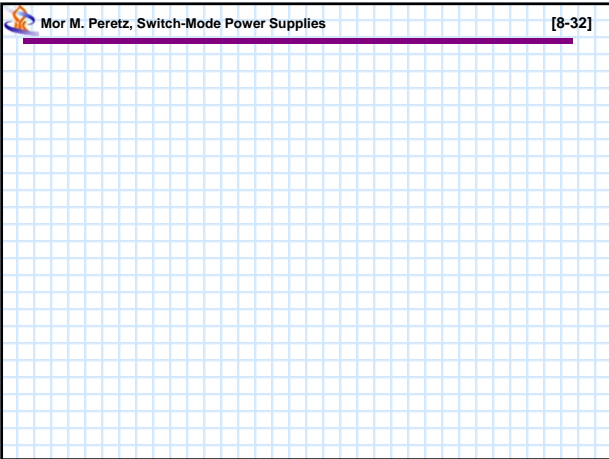

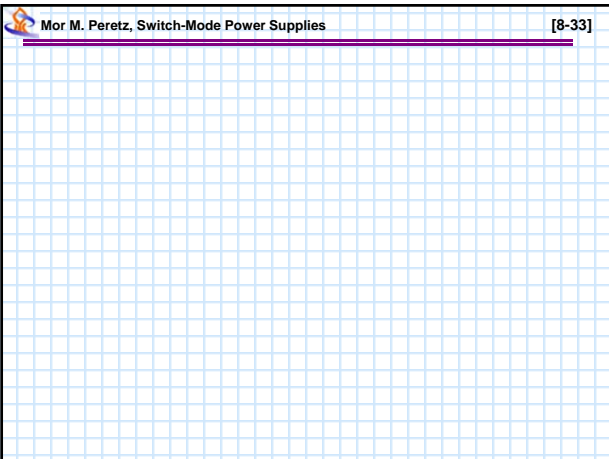


 Mor M. Peretz, Switch-Mode Power Supplies [5-34]

