




Control of switch-mode converters

Current Programmed Mode control CPM



Problem of voltage mode control

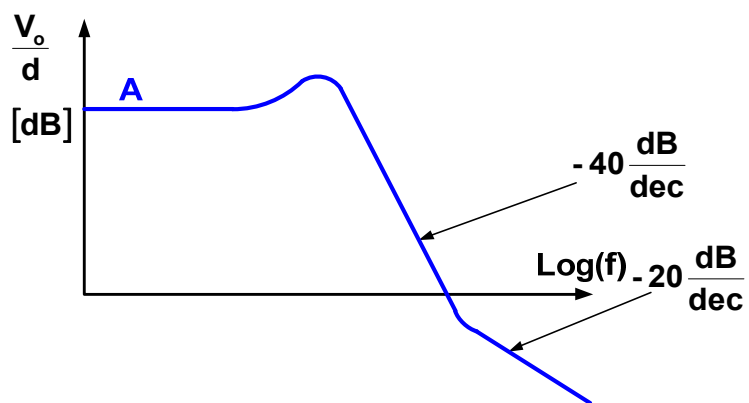


Second order transfer function = complex compensator





Additional feedback System order reduction

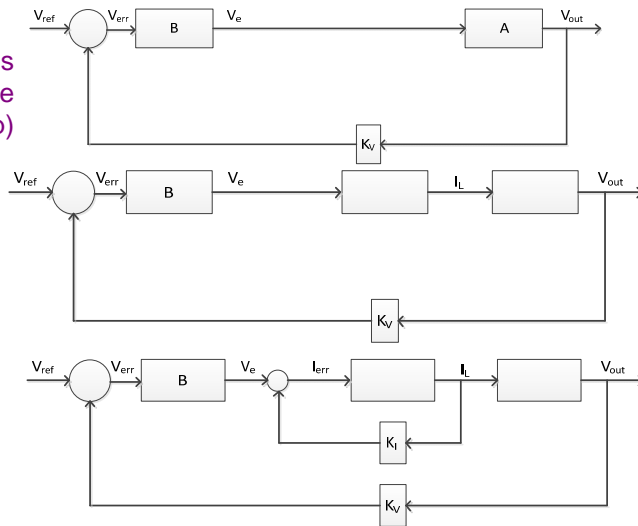System order is reduced for each state variable (inner loop) feedback



Current feedback loop

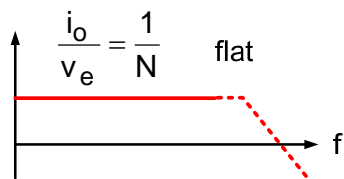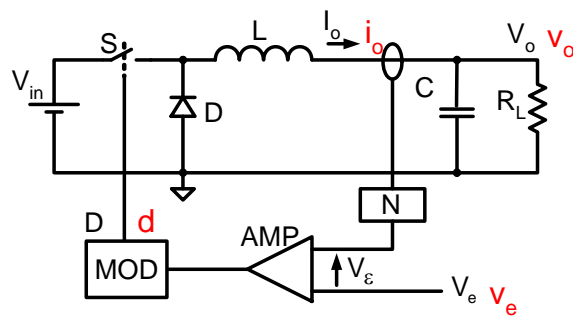



For 'strong' feedback

$$LG \gg 1 \quad v_\epsilon \rightarrow 0$$


$$i_o = \frac{1}{N} v_e$$



System representation in CPM

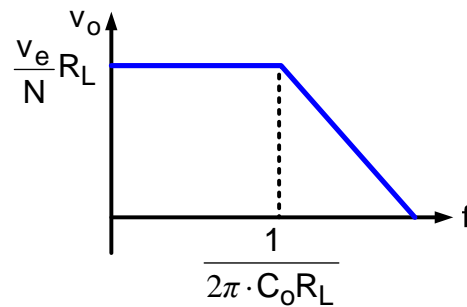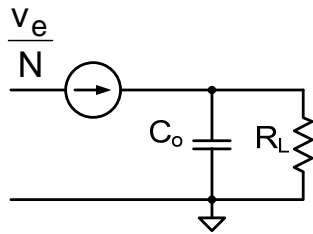


Design of the feedback loops

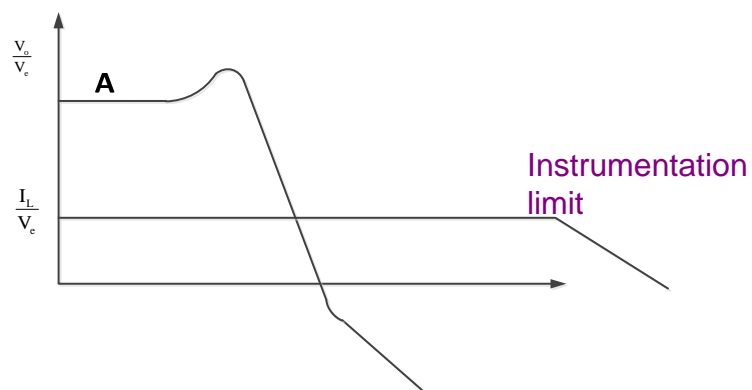


BW of the inner loop must be well above the outer loop BW



Design of the feedback loops

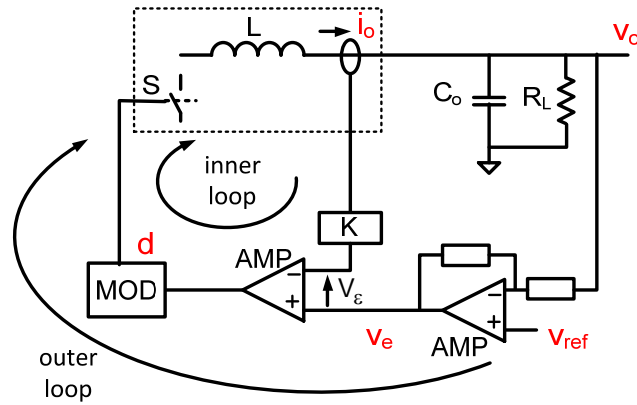

The advantages of current feedback

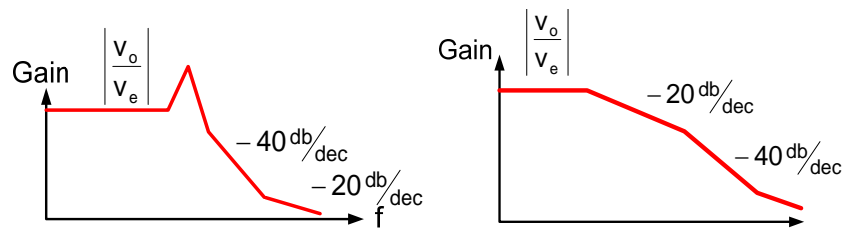


Typical power stage
VM


Same power stage
(outer loop) with
CM



Average current mode

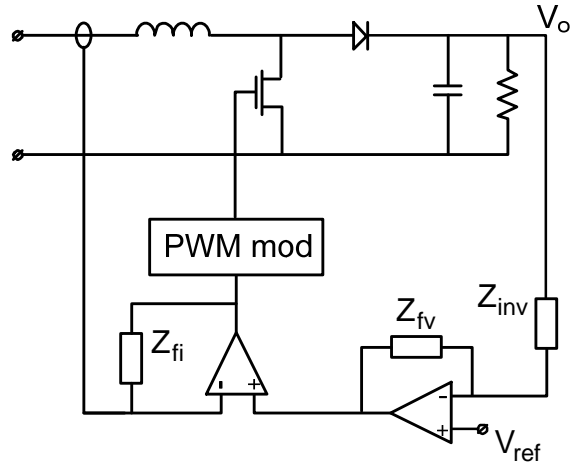

Peak current mode

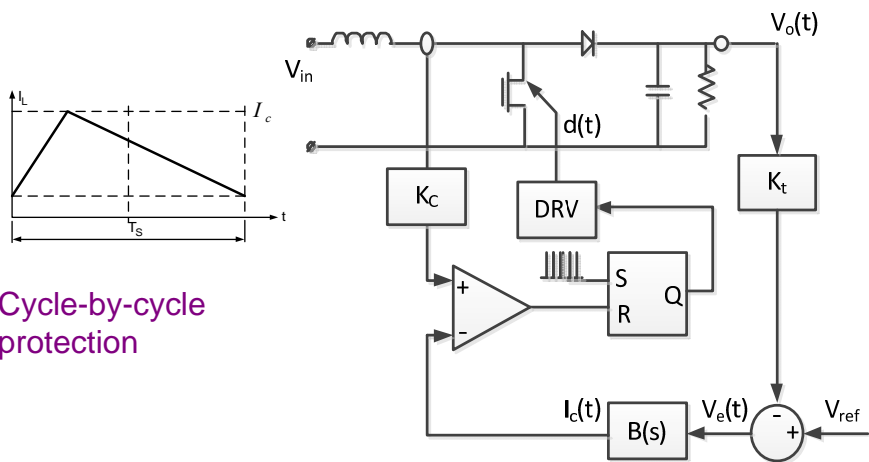




PCM and ACM


- Current feedbacks - reduce the order of system
- The difference is in BW of the current feedback loop
- Increase the output impedance



Sub-harmonic oscillations

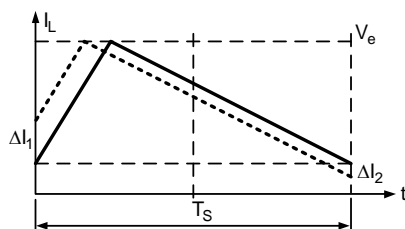

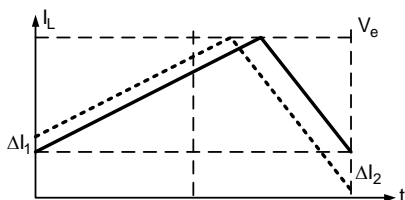
$$D < 0.5 \quad \Delta I_2 < \Delta I_1$$



$$D > 0.5 \quad \Delta I_2 > \Delta I_1$$



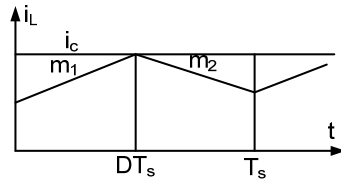Stability analysis of Sub-harmonic oscillations



$$I_L(t_{on}) = I_L(0) + m_1 t_{on}$$

$$I_L(T_s) = I_L(t_{on}) - m_2 t_{off}$$

$$I_L(T_s) = I_L(0) + m_1 t_{on} - m_2 t_{off}$$


Steady-state: $I_L(T_s) = I_L(0)$

$$m_1 t_{on} = m_2 t_{off}$$

$$\frac{t_{on}}{t_{off}} = \frac{m_2}{m_1} = \frac{D_{on}}{D_{off}}$$



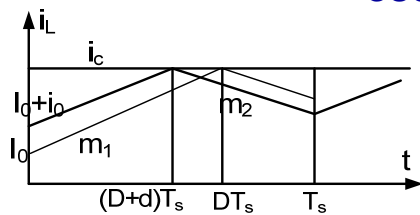Stability analysis of Sub-harmonic oscillations



$$I_L((D+d)T_s) = I_L(0) + i_L(0) + m_1(D+d)T_s$$

$$DC: I_L(DT_s) = I_L(0) + m_1 DT_s$$

$$AC: I_L(dT_s) = i_L(0) + m_1 dT_s$$


$$i_L(0) = -m_1 dT_s$$

$$i_L(T_s) = m_2 dT_s$$

$$i_L(T_s) = i_L(0) \left(-\frac{m_2}{m_1} \right) = i_L(0) \left(-\frac{D_{on}}{D_{off}} \right)$$



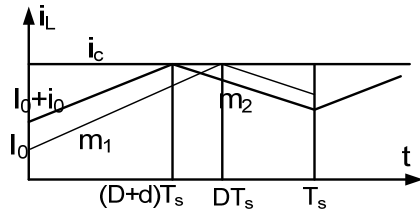Stability analysis of Sub-harmonic oscillations



$$i_L(T_s) = i_L(0) \left(-\frac{D_{on}}{D_{off}} \right)$$


$$i_L(2T_s) = i_L(T_s) \left(-\frac{D_{on}}{D_{off}} \right) = i_L(0) \left(-\frac{D_{on}}{D_{off}} \right)^2$$

$$i_L(nT_s) = i_L((n-1)T_s) \left(-\frac{D_{on}}{D_{off}} \right) = i_L(0) \left(-\frac{D_{on}}{D_{off}} \right)^n$$

$$i_L(nT_s) = i_L(0) \left(-\frac{D_{on}}{D_{off}} \right)^n \quad i_L(nT_s) = \begin{cases} 0, \left| \frac{D_{on}}{D_{off}} \right| < 1 \\ \infty, \left| \frac{D_{on}}{D_{off}} \right| > 1 \end{cases} \rightarrow \text{Stable when } D_{on} < 0.5$$




Slope compensation

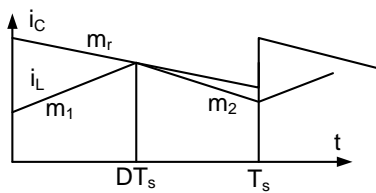


$$I_L(t) + I_r(t) = I_c$$

$$I_L(t) = I_c - I_r(t)$$

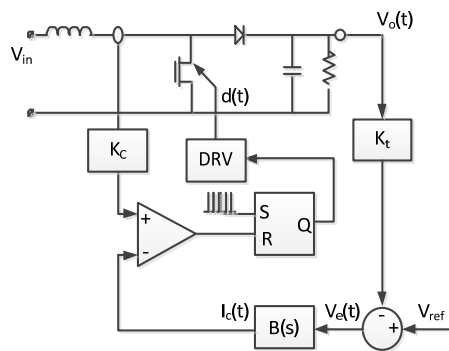



Slope compensation

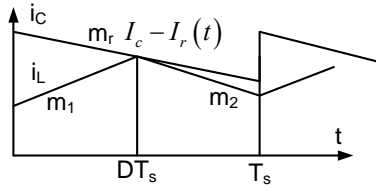

$$i_L(0) = -(m_1 + m_r) dT_s$$

$$i_L(T) = -(m_r - m_2) dT_s$$


$$i_L(T_s) = i_L(0) \left(-\frac{m_2 - m_r}{m_1 + m_r} \right)$$


$$i_L(nT_s) = i_L(0) \left(-\frac{m_2 - m_r}{m_1 + m_r} \right)^n \equiv i_L(0) \alpha^n$$


$$i_L(nT_s) = \begin{cases} 0, & |\alpha| < 1 \\ \infty, & |\alpha| > 1 \end{cases}$$

$$\alpha = -\frac{m_2 - m_r}{m_1 + m_r} = -\frac{1 - \frac{m_r}{m_2}}{\frac{m_1}{m_2} + \frac{m_r}{m_2}} = -\frac{1 - \frac{m_r}{m_2}}{\frac{D_{on} + \frac{m_r}{m_2}}{D_{off} + \frac{m_r}{m_2}}} \rightarrow \frac{m_r}{m_2} \geq 0.5$$



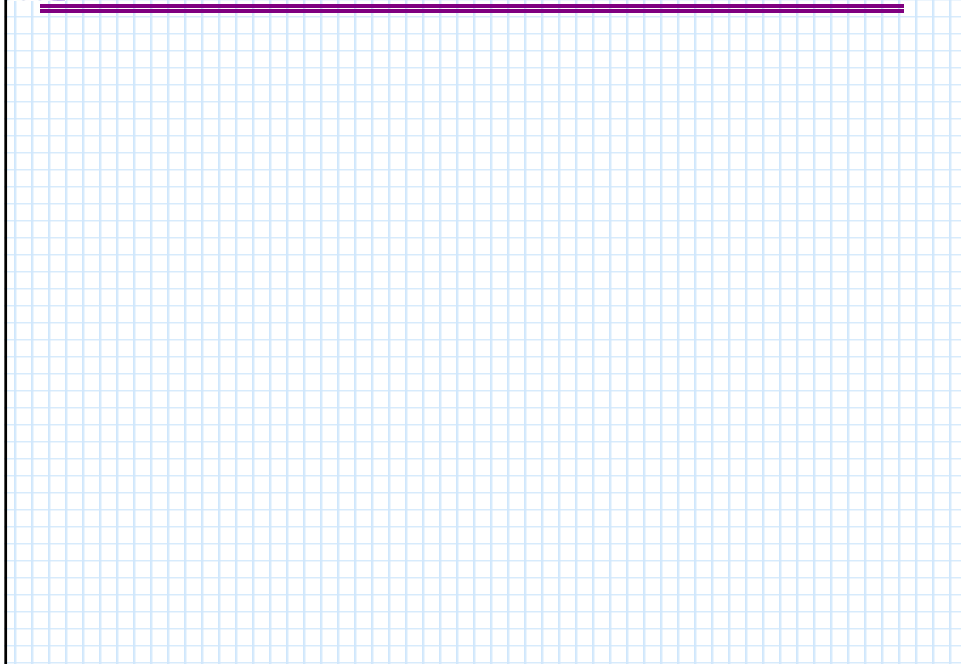 **Mor M. Peretz, Switch-Mode Power Supplies** **[9-19]**



 **Mor M. Peretz, Switch-Mode Power Supplies** **[5-20]**

