

Mor M. Peretz, Switch-Mode Power Supplies [9-1]

Control of switch-mode converters

Current Programmed Mode control CPM

Mor M. Peretz, Switch-Mode Power Supplies [9-2]

Problem of voltage mode control

Second order transfer function = complex compensator

Mor M. Peretz, Switch-Mode Power Supplies [9-3]

Additional feedback System order reduction

System order is reduced for each state variable (inner loop feedback)

Mor M. Peretz, Switch-Mode Power Supplies [9-4]

Current feedback loop

For 'strong' feedback
 $LG \gg 1 \quad v_e \rightarrow 0$
 $i_o = \frac{1}{N} v_e$


Mor M. Peretz, Switch-Mode Power Supplies [9-5]


System representation in CPM


Mor M. Peretz, Switch-Mode Power Supplies [9-6]

Design of the feedback loops

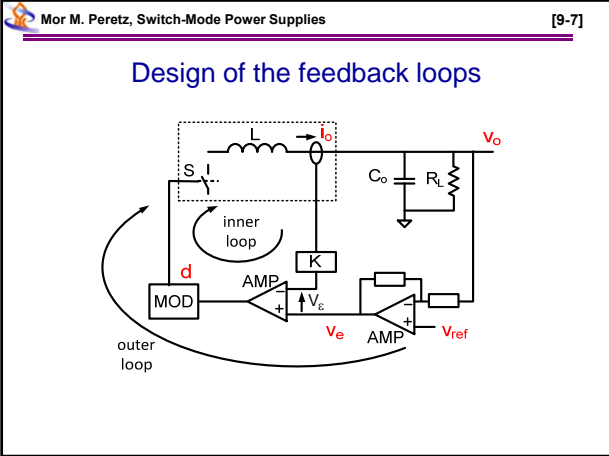BW of the inner loop must be well above the outer loop BW



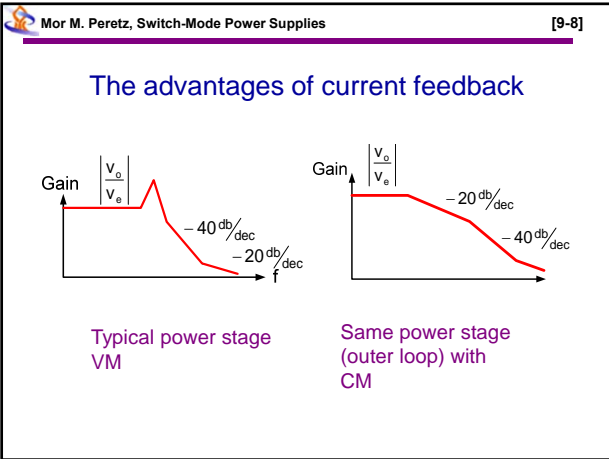

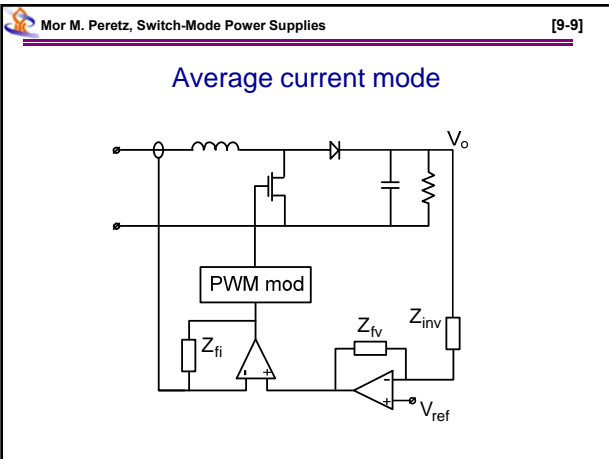

Mor M. Peretz, Switch-Mode Power Supplies [9-10]

Peak current mode

Cycle-by-cycle protection

Mor M. Peretz, Switch-Mode Power Supplies [9-11]

PCM and ACM

- Current feedbacks - reduce the order of system
- The difference is in BW of the current feedback loop
- Increase the output impedance

Mor M. Peretz, Switch-Mode Power Supplies [9-12]

Sub-harmonic oscillations

$D < 0.5 \Delta I_2 < \Delta I_1$

$D > 0.5 \Delta I_2 > \Delta I_1$

Mor M. Peretz, Switch-Mode Power Supplies [9-13]

Stability analysis of Sub-harmonic oscillations

$$I_L(t_{on}) = I_L(0) + m_1 t_{on}$$

$$I_L(T_s) = I_L(t_{on}) - m_2 t_{off}$$

$$I_L(T_s) = I_L(0) + m_1 t_{on} - m_2 t_{off}$$

Steady-state: $I_L(T_s) = I_L(0)$

$$m_1 t_{on} = m_2 t_{off}$$

$$\frac{t_{on}}{t_{off}} = \frac{m_2}{m_1} = \frac{D_{on}}{D_{off}}$$

Mor M. Peretz, Switch-Mode Power Supplies [9-14]

Stability analysis of Sub-harmonic oscillations

$$I_L((D+d)T_s) = I_L(0) + i_L(0) + m_1(D+d)T_s$$

$$DC: I_L(DT_s) = I_L(0) + m_1DT_s$$

$$AC: I_L(dT_s) = i_L(0) + m_1dT_s$$

$$i_L(0) = -m_1dT_s$$

$$i_L(T_s) = m_2dT_s$$

$$i_L(T_s) = i_L(0) \left(-\frac{m_2}{m_1} \right) = i_L(0) \left(-\frac{D_{on}}{D_{off}} \right)$$

Mor M. Peretz, Switch-Mode Power Supplies [9-15]

Stability analysis of Sub-harmonic oscillations

$$i_L(T_s) = i_L(0) \left(-\frac{D_{on}}{D_{off}} \right)$$

$$i_L(2T_s) = i_L(T_s) \left(-\frac{D_{on}}{D_{off}} \right) = i_L(0) \left(-\frac{D_{on}}{D_{off}} \right)^2$$

$$i_L(nT_s) = i_L((n-1)T_s) \left(-\frac{D_{on}}{D_{off}} \right) = i_L(0) \left(-\frac{D_{on}}{D_{off}} \right)^n$$

$$i_L(nT_s) = i_L(0) \left(-\frac{D_{on}}{D_{off}} \right)^n \quad i_L(nT_s) = \begin{cases} 0, \left| \frac{D_{on}}{D_{off}} \right| < 1 \\ \infty, \left| \frac{D_{on}}{D_{off}} \right| > 1 \end{cases} \rightarrow \text{Stable when } D_{on} < 0.5$$

Mor M. Peretz, Switch-Mode Power Supplies [9-16]

Slope compensation

$I_L(t) + I_r(t) = I_c$
 $I_L(t) = I_c - I_r(t)$

Mor M. Peretz, Switch-Mode Power Supplies [9-17]

Slope compensation

$i_L(0) = -(m_1 + m_r)dT_s$
 $i_L(T) = -(m_r - m_2)dT_s$
 $i_L(T_s) = i_L(0) \left(\frac{m_2 - m_r}{m_1 + m_r} \right)$


$i_L(nT_s) = i_L(0) \left(\frac{m_2 - m_r}{m_1 + m_r} \right)^n \equiv i_L(0) \alpha^n$

$i_L(nT_s) = \begin{cases} 0, & |\alpha| < 1 \\ \infty, & |\alpha| > 1 \end{cases}$

$\alpha = -\frac{m_2 - m_r}{m_1 + m_r} = -\frac{1 - \frac{m_r}{m_2}}{\frac{m_1}{m_2} + \frac{m_r}{m_2}} = -\frac{D_{on} - \frac{m_r}{m_2}}{D_{off} + \frac{m_r}{m_2}} \rightarrow \frac{m_r}{m_2} \geq 0.5$

Mor M. Peretz, Switch-Mode Power Supplies [9-18]

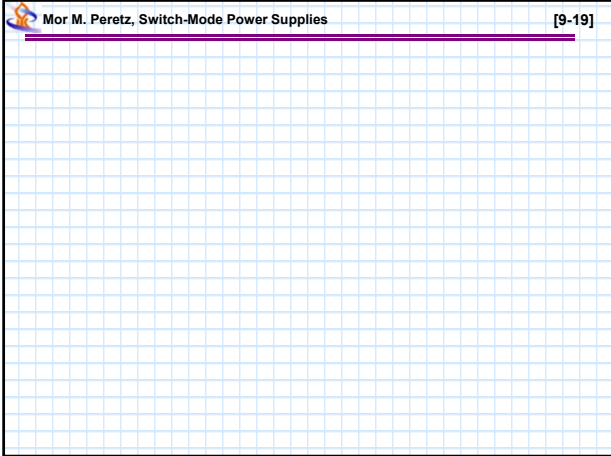Mor M. Peretz, Switch-Mode Power Supplies [9-19]



Mor M. Peretz, Switch-Mode Power Supplies [5-20]

